

Al's Electronic Class Room



Understanding Voltage

AC Voltage



- AC Voltage Current flows in Both Directions.
- The Voltage that is brought into our home, 120 RMS VAC at 60 Hz
- Easier to transport over long distance Then DC Voltage

Al's Electronic Class Room


Understanding Voltage



Understanding Voltage

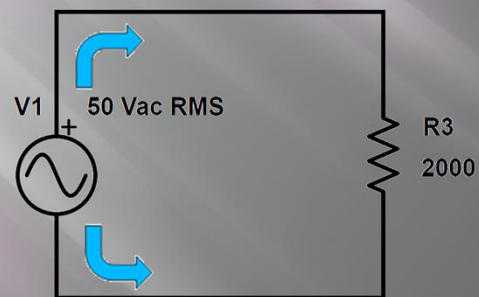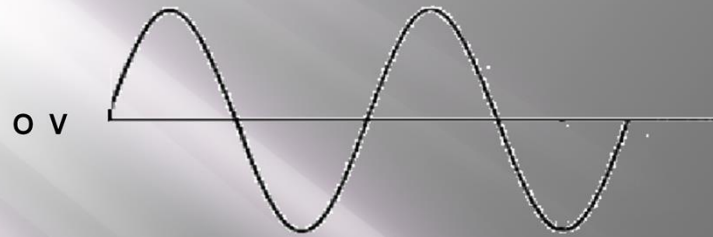

Understanding Voltage

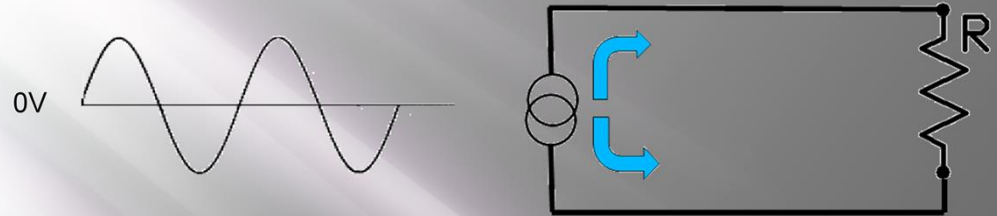

- The hertz (symbol: Hz) is the derived unit of frequency is defined as one cycle per second.
- It is named for Heinrich Rudolf Hertz, the first person to provide conclusive proof of the existence of electromagnetic waves.
- Hertz are commonly expressed in multiples: kilohertz (kHz), megahertz(MHz),gigahertz (GHz), and terahertz (THz).

Understanding Voltage


What is RMS Voltage AC ?

Root-Mean-Square

- Take The Square of each Individual Value (Square).
- Adding the Squares Dividing the Sum by the Number of Values (Mean).
- Take the Square Root of this Value is the RMS Value (Root)

Al's Electronic Class Room

Understanding Voltage

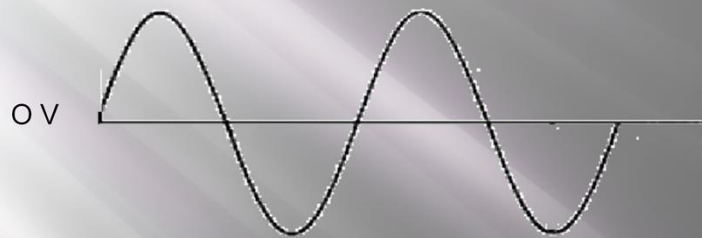

Understanding Voltage,

What is RMS Voltage AC ?


Root-Mean-Square

Example: Find the RMS Value of 2,3,4

- Take The Square of Each Value $2^2 = 4$, $3^2 = 9$, $4^2 = 16$
- Find the Mean (Average) , $4 + 9 + 16 / 3 = 29/3 = 9.67$
- Root Square Root of 9.67, $\sqrt{9.67} = \text{RMS Value } 3.11$

Al's Electronic Class Room

Understanding Voltage

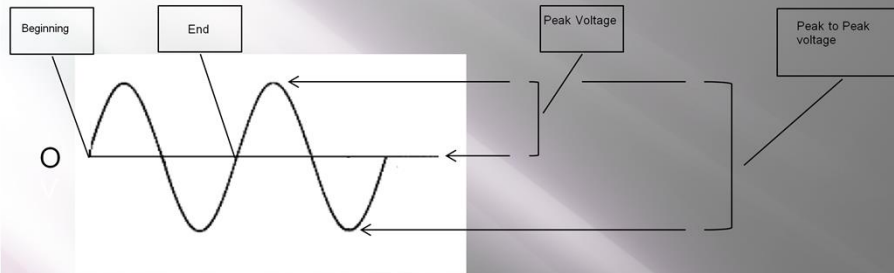

- 120 VAC RMS at 60 Hz.
- Peak Voltage Equals $1.414 \times \text{RMS}$
- Peak to Peak Voltage equals $2.828 \times \text{RMS}$ or $2 \times \text{Peak Voltage}$
- RMS Voltage Equals $.707 \times \text{Peak Voltage}$
- $1/T = F$ & $1/F = T$

Understanding Voltage

- 120 VAC RMS at 60 Hz.
- Peak Voltage Equals $1.414 \times \text{RMS}$
- Peak to Peak Voltage equals $2.828 \times \text{RMS}$ or $2 \times \text{Peak Voltage}$
- RMS Voltage Equals $.707 \times \text{Peak Voltage}$
- $1/T = F$ & $1/F = T$

Questions

- 60 VAC Find p-p Voltage =
- 90 VAC p-p Find Peak Voltage =
- 170 VAC Peak Find RMS =
- Find T for 60 Hz =
- Find F for 8.33 ms =


Understanding Voltage

- 120 VAC RMS at 60 Hz.
- Peak Voltage Equals $1.414 \times \text{RMS}$
- Peak to Peak Voltage equals $2.828 \times \text{RMS}$ or $2 \times \text{Peak Voltage}$
- RMS Voltage Equals $.707 \times \text{Peak Voltage}$
- $1/T = F$ & $1/F = T$

Answers to Questions

- 60 VAC Find p-p Voltage = 169.68 or 170 Volts p-p AC
- 90 VAC p-p Find Peak Voltage = 45 Volts Peak AC
- 170 VAC Peak Find RMS = 120.19 Volts AC
- Find T for 60 Hz = 0.01667 s or 16.67 ms
- Find F for 8.33 ms = 120 Hz

Understanding Voltage

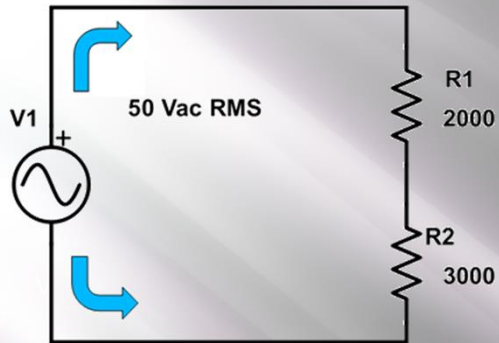


$$V_{R1} = V_1 \left(\frac{R_1}{R_1 + R_2} \right) ; 50 \text{ Vac} \left(\frac{2000}{5000} \right)$$

$$V_{R1} = 20 \text{ Vac RMS.}$$

$$V_{R2} = V_1 - V_{R1} = 50 \text{ Vac} - 20 \text{ Vac} = 30 \text{ Vac}$$
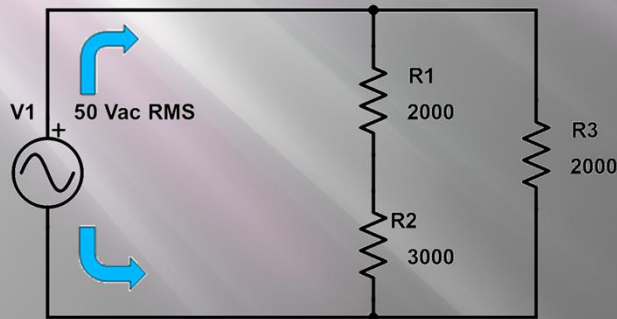
$$I_{\text{Total}} = V_1 / R_T = 50 \text{ Vac} / 5000 = 10 \text{ ma}$$



$$V_{R1} = V_1 \left(\frac{R_1}{R_1 + R_2} \right) ; 50 \text{ Vac} \left(\frac{2000}{5000} \right)$$

$$V_{R1} = 20 \text{ Vac RMS.}$$

$$V_{R2} = V_1 - V_{R1} = 50 \text{ Vac} - 20 \text{ Vac} = 30 \text{ Vac}$$

$$R_T = R_1 + R_2 \parallel R_3 = 5000 \parallel 2000 = 1428 \text{ ohms}$$

$$I_1 = V_1 / R_1 + R_2 = 50 \text{ Vac} / 5000 =$$

Understanding Voltage

Conversions:

1 Volt = 1000 milli Volts or 1000000 u Volts or Micro Volts;

Powers of 10; 1×10^{-3} is milli; 1×10^{-6} μ or micro

1000 Volts = 1 Kilo Volts ; 1 KV Powers of 10 : $1 \times 10^{+3}$

1000000 Volts = 1 Mega Volts : Powers of 10 : $1 \times 10^{+6}$

Al's Electronic Class Room

Al's Electronic Class Room



Capacitance

- Capacitors have two Metal plates as shown in the diagram
- Dielectric Material (which is a type of insulator is placed in between the plates).
- Types of Dielectric Materials are air, Mica or Paper.
- Free Electrons cannot flow thru a insulator the Capacitor holds a charge.

Schematic Symbols of a Capacitor



Non Polarized



Polarized



Variable

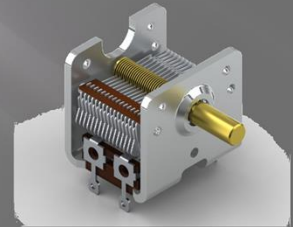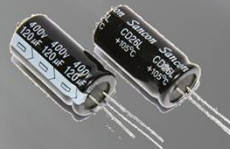

Al's Electronic Class Room

Capacitance

15 Vdc



Type of Dielectrics:

DIELECTRIC MATERIALS
Air
Alsimag 196
Bakelite
Cellulose
Fiber
Formica
Glass
Mica
Mycalox
Paper
Plexiglass
Polyethylene
Polystyrene
Porcelain
Pyrex
Quartz
Steatite
Teflon

- Capacitor will Charge instantly
- The Voltage Across the Capacitor Equals the Voltage Source.
- Electrons are redistributed on the Capacitor

Charge on the Capacitor is $Q=CV$

Where: Q is Coulombs

C is the Value Of Capacitance Measured in Farads

V is the voltage across the capacitor

Al's Electronic Class Room

Capacitance

- Capacitors have two Metal plates as shown in the diagram
- Dielectric Material (which is a type of insulator is placed in between the plates).
- Types of Dielectric Materials are air, Mica or Paper.
- Free Electrons cannot flow thru a insulator the Capacitor holds a charge.



Charge on the Capacitor is $Q=CV$

Where: Q is Coulombs

C is the Value Of Capacitance Measured in Farads

V is the voltage across the capacitor

1 Coulomb of Charge is defined of having an imbalance of Electrons on a capacitor of 6.25×10^{18} Electrons.

Capacitors are measured in Micro Farads Abbreviated μf (10^{-6}) & Pico Farads pF (10^{-12}), Also Capacitors have a working Voltage rating. Ex 47 μf 50WVDC

Al's Electronic Class Room

Capacitance

- Capacitors have two Metal plates as shown in the diagram
- Dielectric Material (which is a type of insulator is placed in between the plates).
- Types of Dielectric Materials are air, Mica or Paper.
- Free Electrons cannot flow thru a insulator the Capacitor holds a charge.

15 Vdc



Dielectric

1 Coulomb of Charge is defined of having an imbalance of Electrons on a capacitor of 6.25×10^{18} Electrons.

Capacitors are measured in Micro Farads Abbreviated μf (10^{-6}) & Pico Farads nF (10^{-12})

Charge on the Capacitor is $Q=CV$

Where: Q is Coulombs

C is the Value Of Capacitance Measured in Farads

V is the voltage across the capacitor

Problem: Charge Stored In a 2 μF capacitor at 50 VDC across it.

$$Q = 2 \times 10^{-6} \times 50 \text{ VDC} = 100 \times 10^{-6} = 100 \times 10^{-6} \text{ Coulombs}$$

Problem: Charge Stored In a 2 μF capacitor at 50 VDC across it.

$$Q = 40 \times 10^{-6} \times 50 \text{ VDC} = 2000 \times 10^{-6} = 2000 \times 10^{-6} \text{ Coulombs}$$

Al's Electronic Class Room

Capacitance

- Capacitors have two Metal plates as shown in the diagram
- Dielectric Material (which is a type of insulator is placed in between the plates).
- Types of Dielectric Materials are air, Mica or Paper.
- Free Electrons cannot flow thru a insulator the Capacitor holds a charge.

15 Vdc



Dielectric

1 Coulomb of Charge is defined of having an imbalance of Electrons on a capacitor of 6.25×10^{18} Electrons.

Capacitors are measured in Micro Farads Abbreviated μf (10^{-6}) & Pico Farads nF (10^{-12})

Charge on the Capacitor is $Q=CV$

Where: Q is Coulombs

C is the Value Of Capacitance Measured in Farads

V is the voltage across the capacitor

$$I = Q/t$$

Where: I is Current

t is Time

Q is Charge in Coulombs

Problem:

2 μA of Current Charges a Capacitor for 20 Seconds

Find Q: $Q = I \times t$; $2 \times 10^{-6} \times 20 = 40 \times 10$ or 40 μC

Al's Electronic Class Room

Capacitance

Schematic Symbols of a Capacitor



Dielectric

1 Coulomb of Charge is defined of having an imbalance of Electrons on a capacitor of 6.25×10^{18} Electrons.

Capacitors are measured in Micro Farads Abbreviated μf (10^{-6}) & Pico Farads nF (10^{-12})

$$I = Q/t$$

Where: I is Current

t is Time

Q is Charge in Coulombs

Charge on the Capacitor is $Q=CV$

Where: Q is Coulombs

C is the Value Of Capacitance Measured in Farads

V is the voltage across the capacitor

Problem:

2 μA of Current Charges a Capacitor for 20 Seconds

Find Q: $Q = I \times t$; $2 \times 10^{-6} \times 20 = 40 \times 10$ or $40 \mu\text{C}$

Find value of Capacitance from above Problem; $v = 20 \text{ Vdc}$

$C = Q/V$; $40 \times 10^{-6} / 20 \text{ Vdc} = 2 \times 10^{-6}$; $2 \mu\text{F}$

Current of 5 ma Charges a $10 \mu\text{f}$ for 1 sec. Find V across the Capacitor: $Q = I \times t$; $5 \times 10^{-3} \times 1 = 5 \times 10^{-3}$ Coulombs.


$Q/C = V$; $5 \times 10^{-3} / 10 \times 10^{-6} = 0.5 \times 10^3$ 500 volts

Al's Electronic Class Room

Capacitance


- Capacitors in Series add Indirectly
C1= 10 uF ; C2 = 10 uF ; C3 = 5 uF
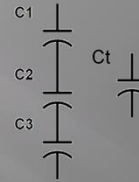
$$\frac{1}{\frac{1}{C1} + \frac{1}{C2} + \frac{1}{C3}} = \frac{1}{\frac{1}{10 \times 10^{-6}} + \frac{1}{10 \times 10^{-6}} + \frac{1}{5 \times 10^{-6}}} = 2.5 \text{ uf}$$



- Capacitors in Parallel add directly
C1= 10 uF ; C2 = 10 uF ; C3 = 5 uF
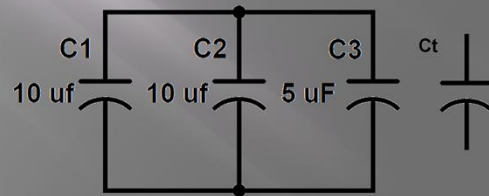
$$C1 + C2 + C3 = Ct$$
$$10 \text{ uf} + 10 \text{ uf} + 5 \text{ uf} = 25 \text{ uf}$$



Al's Electronic Class Room


Al's Electronic Class Room



Capacitance

$$\frac{1}{2\pi fc} = X_c ; \pi = 3.14$$

Capacitance Reactance

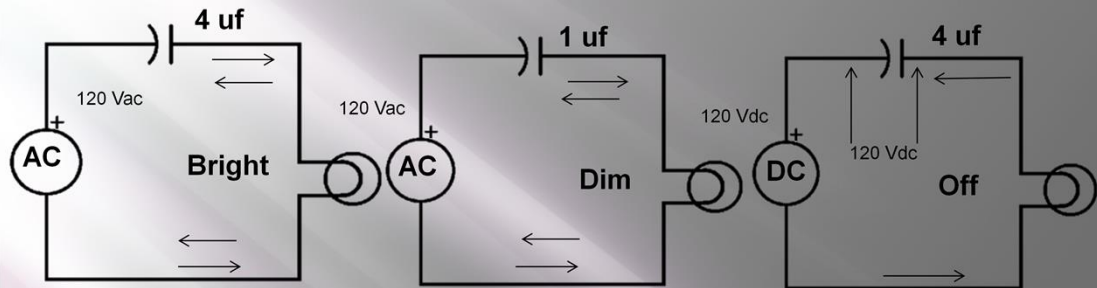

$$\frac{1}{2\pi fc} = \frac{1}{6.28 (60)(4 \times 10^{-6})} = 663 \Omega$$

$$\frac{1}{2\pi fc} = \frac{1}{6.28 (60)(1 \times 10^{-6})} = 2652 \Omega$$



Open Circuit

- Alternating current flows in a capacitive circuit with ac voltage applied.
- A smaller capacitance allows less current, which means more X_c with more ohms of opposition.
- Lower Frequencies for the applied voltage results in less current and more X_c . With DC voltage which has a frequency of "0" X_c is infinite and no current flows in circuit.

Al's Electronic Class Room

Capacitance

Capacitance Reactance

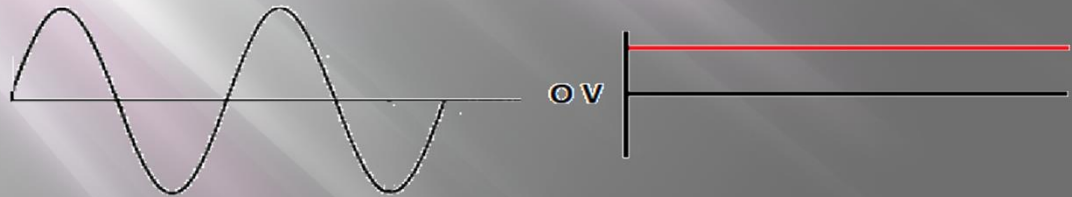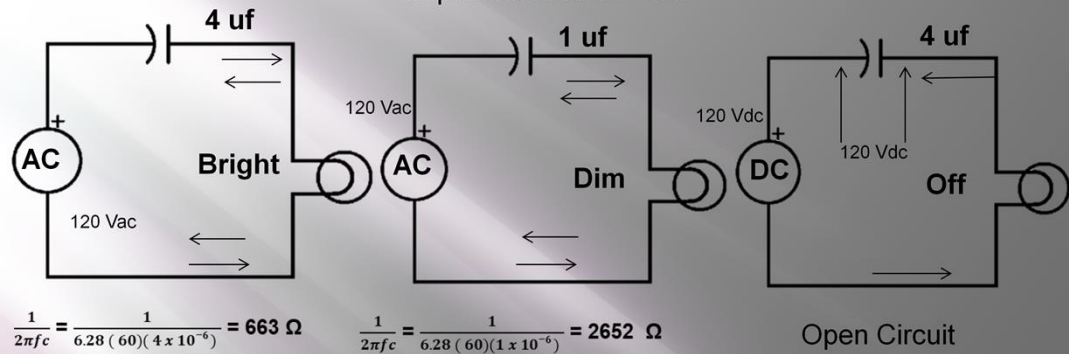

Al's Electronic Class Room

Capacitance

Capacitance Reactance

$$X_c = \frac{1}{2\pi f c}; \frac{1}{(6.28)fc} = \left(\frac{0.159}{1}\right)\left(\frac{1}{fc}\right) = \frac{0.159}{fc} \quad \bullet \quad \text{Frequency } f \text{ \& } \text{Capacitance } C \text{ are Inversely Proportional to } X_c$$

Problems: Find X_c

- $C = 0.1 \mu f, f = 1000 \text{ Hz} \quad X_c = ?$
- $C = 1 \mu f, f = 1000 \text{ Hz} \quad X_c = ?$
- $C = 100 \text{ pf}, f = 1 \text{ MHz} \quad X_c = ?$
- $C = 100 \text{ pf}, f = 10 \text{ MHz} \quad X_c = ?$
- $C = 240 \text{ pf}, f = 41.67 \text{ KHz} \quad X_c = ?$

Al's Electronic Class Room

Capacitance

Capacitance Reactance

$$X_c = \frac{1}{2\pi f c}; \frac{1}{(6.28)fc} = \left(\frac{0.159}{1}\right)\left(\frac{1}{fc}\right) = \frac{0.159}{fc} \quad \bullet \quad \text{Frequency } f \text{ \& } \text{Capacitance } C \text{ are Inversely Proportional to } X_c$$

Problems: Find X_c

- $C = 0.1 \mu f, f = 1000 \text{ Hz} \quad X_c = 1591 \, \Omega$
- $C = 1 \mu f, f = 1000 \text{ Hz} \quad X_c = 159 \, \Omega$
- $C = 100 \text{ pf}, f = 1 \text{ MHz} \quad X_c = 1591 \, \Omega$
- $C = 100 \text{ pf}, f = 10 \text{ MHz} \quad X_c = 159 \, \Omega$
- $C = 240 \text{ pf}, f = 41.67 \text{ KHz} \quad X_c = 15914 \, \Omega$

Al's Electronic Class Room

Capacitance


Capacitance Reactance

- Capacitors Reactance in Series add directly

$C1 = 10 \mu F$; $C2 = 10 \mu F$; $C3 = 5 \mu F$; 100 Hz

$$X_{c1} + X_{c2} + X_{c3} = X_{ct} ; 159 \Omega + 159 \Omega + 318 \Omega = 636 \Omega$$

$$C_t = 636 \Omega$$

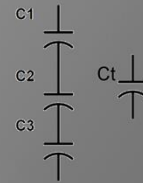


- Capacitors in Parallel add indirectly

$C1 = 10 \mu F$; $C2 = 10 \mu F$; $C3 = 5 \mu F$

$$C1 + C2 + C3 = C_t$$

$$10 \mu F + 10 \mu F + 5 \mu F = 25 \mu F$$
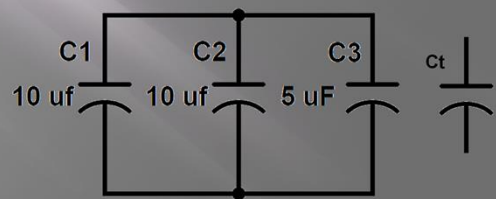
$$\frac{1}{\frac{1}{X_{c1}} + \frac{1}{X_{c2}} + \frac{1}{X_{c3}}} = \frac{1}{\frac{1}{159 \Omega} + \frac{1}{159 \Omega} + \frac{1}{318 \Omega}} = 63.6 \Omega$$




$$C_t = 63.6 \Omega$$


Al's Electronic Class Room

Capacitance

Capacitance Reactance

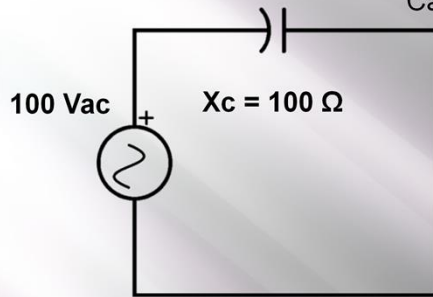
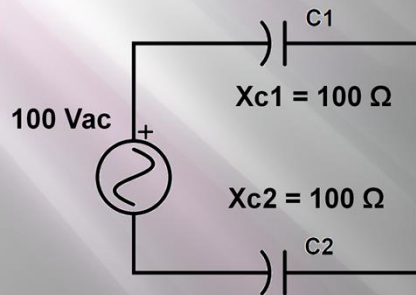
$$I_{ac} = \frac{VAC}{X_{C1}} = \frac{100 VAC}{100 \Omega} = 1 A_{ac}$$




$$I_{ac} = \frac{VAC}{X_{C1} + X_{C2}} = \frac{100 VAC}{200 \Omega} = 0.5 A_{ac}$$


Al's Electronic Class Room

Capacitance



Current & Voltage are in Phase

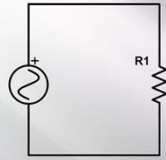

Capacitance Reactance

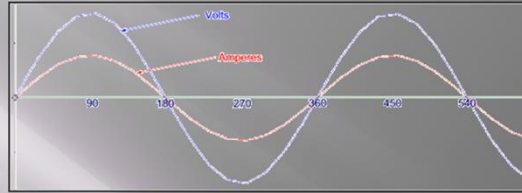

Current leads Voltage by 90°

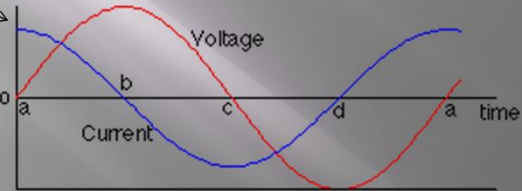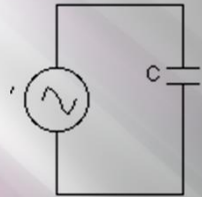

Voltage

- a. 0°
- b. 90°
- c. 180°
- d. 270°

Current

- a. 90°
- b. 180°
- c. 270°
- d. 0°

Al's Electronic Class Room


Al's Electronic Class Room




Capacitance

Capacitance Reactance
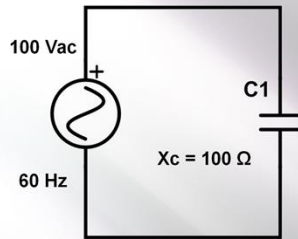
$$I_{ac} = \frac{V_{ac}}{X_{C1}} = \frac{100 V_{ac}}{100 \Omega} = 1 ac Amp$$



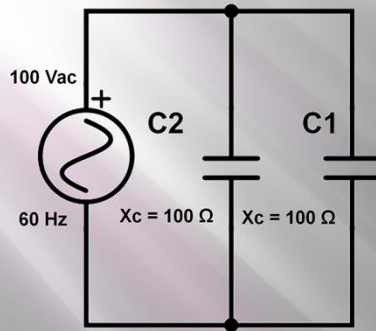- Capacitive Series Circuit I is the Same
- Voltage is the same across the capacitors
- Frequency is the the same for Voltage and Current






$$I_{ac} = \frac{V_{ac}}{X_{ct}} = \frac{100 V_{ac}}{50 \Omega} = 2 ac Amp$$

Al's Electronic Class Room

Capacitance=


Capacitance Reactance

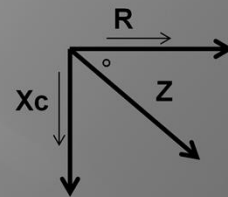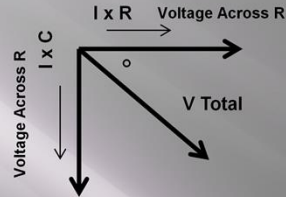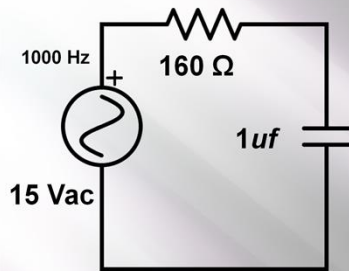



- $X_c = \frac{1}{2\pi f c} = \frac{1}{6.28 (1000) (1 \times 10^{-6})} \cong 160 \Omega$
- $Z = \sqrt{R^2 + X_c^2} = \sqrt{160^2 + 160^2} = 226 \Omega$
- $I_t = \frac{V_{ac}}{Z} = \frac{15 V_{ac}}{226 \Omega} = 0.0663 \text{ Ac amps}$
- $V_R = 160 \Omega \times 0.0663 \text{ Ac amps} = 10.6 \text{ Vac}$
- $V_c = 160 \Omega \times 0.0663 \text{ Ac amps} = 10.6 \text{ Vac}$
- $V_t = \sqrt{V_R^2 + V_C^2} = \sqrt{10.6^2 + 10.6^2} = \sqrt{224.72} = 14.99 \text{ Vac}$
- Find θ ; $\tan \theta = \frac{X_c}{R} = \frac{160}{160} = 1 = 45^\circ$ (Use $\tan^{-1}$ function on Calculator)

Al's Electronic Class Room

Capacitance

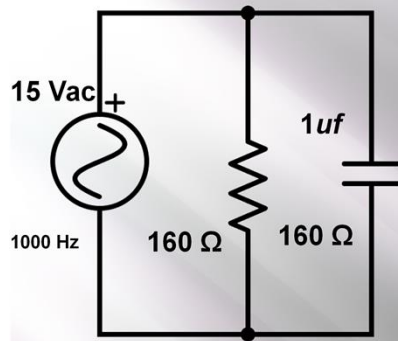

Capacitance Reactance

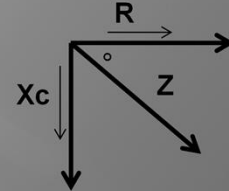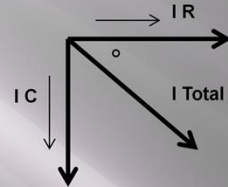


- $X_c = \frac{1}{2\pi f c} = \frac{1}{6.28 (1000)(1 \times 10^{-6})} \cong 160 \Omega$
- $I_C = \frac{V_{ac}}{X_c} = \frac{15 V_{ac}}{160 \Omega} \cong 94 \text{ ma} ; I_R = \frac{15 V_{ac}}{160 \Omega} \cong 94 \text{ MA}$
- $I_t = \sqrt{I_C^2 + I_R^2} = \sqrt{94 \text{ ma}^2 + 94 \text{ ma}^2} \cong 133 \text{ Ma}$
- $Z = \frac{V_{ac}}{I_t} = \frac{15 V_{ac}}{133 \text{ ma}} = 112 \Omega$
- Find θ ; $\tan \theta = \frac{I_c}{I_R} = \frac{94 \text{ ma}}{94 \text{ ma}} = 1 = 45^\circ$ (Use $\tan^{-1}$ function on Calculator)

Al's Electronic Class Room

Capacitance

Capacitance Reactance

Coupling Capacitor C_c

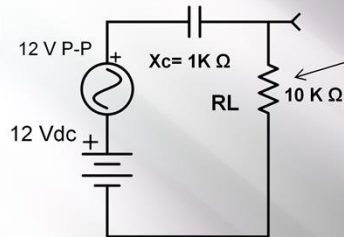

Input Resistance for AC Coupling Amplifier

- Capacitor C_c will block Dc Voltage and allow Ac signal to Pass
- Criteria Pass Frequencies of 100 Hz above.

- X_c wants to be 1/10 of R_L ; $X_c = 1k\Omega$

$$\bullet \quad X_c = \frac{0.159}{f_c} ; C = \frac{0.159}{(X_c)f} = \frac{0.159}{1000 \Omega (100 \text{ Hz})} = \frac{0.159}{100000} = 1.6 \text{ } \mu\text{f @ } 36 \text{ Wvdc}$$

$$\bullet \quad X_c = \frac{0.159}{f_c} = \frac{0.159}{(1000)(1.6 \times 10^{-6})} \cong 100 \Omega$$


Al's Electronic Class Room

Al's Electronic Class Room



Capacitance

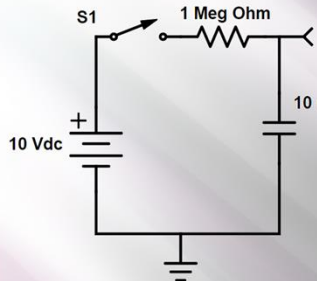Resistor & Capacitor time Constant(s), *RC time constant(s)*




- **RC Time Constants ; $R \times C = \text{time of one time constant.}$**
- **Five time Constant to approximately Charge to Supply Voltage.**
- **Each time Constant Charges to 63 % of Supply Voltage**

$$1 TC = R \times C ; 1 \text{ Meg } \Omega \times 10 \mu\text{f} ; (1 \times 10^6) \times (10 \times 10^{-6})$$

$$1 TC = 10 \text{ Seconds}$$


Time Constant	RC Value	Percentage of Maximum	
		Voltage	Current
0.5 time constant	0.5RC	39.3%	60.7%
0.7 time constant	0.7RC	50.3%	49.7%
1.0 time constant	1RC	63.2%	36.8%
2.0 time constants	2RC	86.5%	13.5%
3.0 time constants	3RC	95.0%	5.0%
4.0 time constants	4RC	98.2%	1.8%
5.0 time constants	5RC	99.3%	0.7%

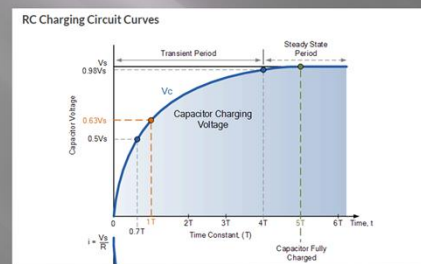

Al's Electronic Class Room

Capacitance

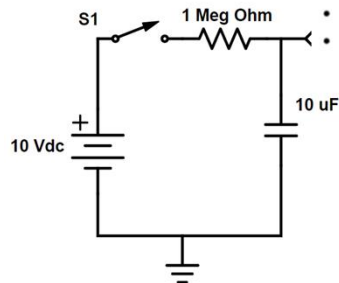Resistor & Capacitor time Constant(s), *RC time constant(s)*




- **RC Time Constants ; $R \times C = \text{time of one time constant.}$**
- **Five time Constant to approximately Charge to Supply Voltage.**
- **Each time Constant Charges to 63 % of Supply Voltage**

$$1 TC = R \times C ; 1 \text{ Meg } \Omega \times 10 \mu\text{f} ; (1 \times 10^6) \times (10 \times 10^{-6})$$

$$1 TC = 10 \text{ Seconds}$$

RC Charging Circuit Curves

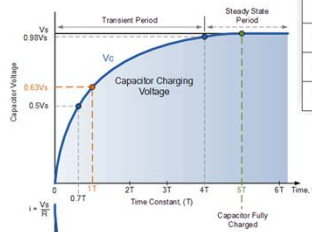


Time Constant	RC Value	Percentage of Maximum	
		Voltage	Current
0.5 time constant	0.5RC	39.3%	60.7%
0.7 time constant	0.7RC	50.3%	49.7%
1.0 time constant	1RC	63.2%	36.8%
2.0 time constants	2RC	86.5%	13.5%
3.0 time constants	3RC	95.0%	5.0%
4.0 time constants	4RC	98.2%	1.8%
5.0 time constants	5RC	99.3%	0.7%

Al's Electronic Class Room

Capacitance

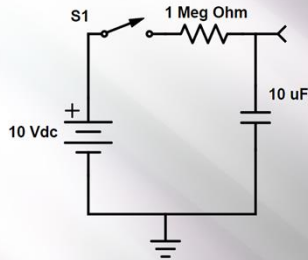Resistor & Capacitor time Constant(s), *RC time constant(s)*



- RC Time Constants ; $R \times C = \text{time of one time constant.}$
- Five time Constant to approximately Charge to Supply Voltage.
- Each time Constant Charges to 63 % of Supply Voltage

$$1 \text{ TC} = R \times C ; 1 \text{ Meg } \Omega \times 1 \text{ uF} ; (1 \times 10^6) \times (10 \times 10^{-6})$$

$$1 \text{ TC} = 10 \text{ Seconds}$$

Voltage Across Capacitor

$$0.5 \text{ TC} \times 10 \text{ Sec} = 5 \text{ Sec} ; 0.393 \times 10 \text{ VDC} = 3.93 \text{ Volts}$$

$$0.7 \text{ TC} \times 10 \text{ Sec} = 7 \text{ Sec} ; 0.503 \times 10 \text{ VDC} = 5.03 \text{ Volts}$$

$$1 \text{ TC} \times 10 \text{ Sec} = 10 \text{ Sec} ; 0.632 \times 10 \text{ VDC} = 6.32 \text{ Volts}$$

$$2 \text{ TC} \times 10 \text{ Sec} = 20 \text{ Sec} ; 0.865 \times 10 \text{ VDC} = 8.65 \text{ Volts}$$

$$3 \text{ TC} \times 10 \text{ Sec} = 30 \text{ Sec} ; 0.95 \times 10 \text{ VDC} = 9.5 \text{ VDC}$$

$$4 \text{ TC} \times 10 \text{ Sec} = 40 \text{ Sec} ; 0.982 \times 10 \text{ VDC} = 9.82 \text{ VDC}$$

$$5 \text{ TC} \times 10 \text{ Sec} = 50 \text{ Sec} ; 0.993 \times 10 \text{ VDC} = 9.93 \text{ VDC}$$

Voltage Across Resistor

$$V_s - V_c = V_R$$

$$10 \text{ Vdc} - 3.94 \text{ VDC} = 6.06 \text{ Vdc}$$

$$10 \text{ Vdc} - 5.03 \text{ VDC} = 4.97 \text{ Vdc}$$


$$10 \text{ Vdc} - 6.32 \text{ VDC} = 3.68 \text{ Vdc}$$

$$10 \text{ Vdc} - 8.65 \text{ VDC} = 1.35 \text{ Vdc}$$

$$10 \text{ Vdc} - 9.5 \text{ VDC} = 0.5 \text{ Vdc}$$

$$10 \text{ Vdc} - 9.82 \text{ VDC} = 0.18 \text{ Vdc}$$




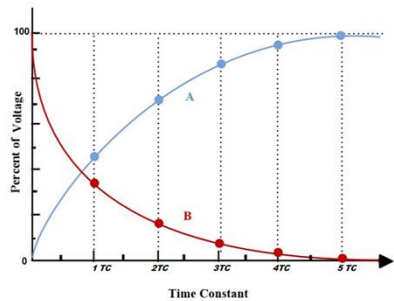
$$10 \text{ Vdc} - 9.93 \text{ VDC} = 0.07 \text{ Vdc}$$



Al's Electronic Class Room

Capacitance

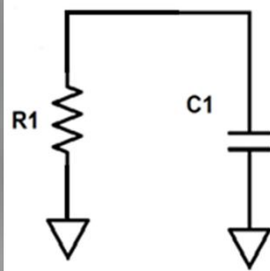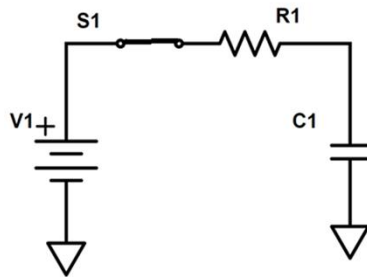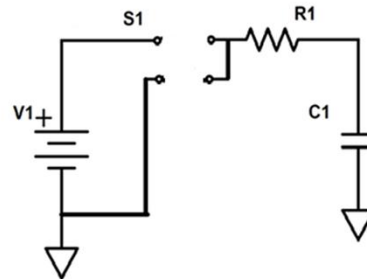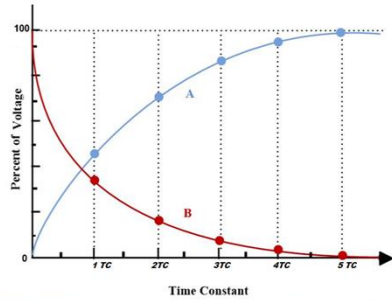Resistor & Capacitor time Constant(s), *RC time constant(s)*



Capacitance


Resistor & Capacitor time Constant(s), *RC time constant(s)*

Where:

- V_c is the voltage across the Capacitor.
- V_s is the supply voltage.
- T is the elapsed time since the application of the supply voltage.
- RC is the *time constant* of the RC charging circuit.

$$V_c = V_s(1 - e^{-t/RC}) \quad \text{Use Calculator}$$
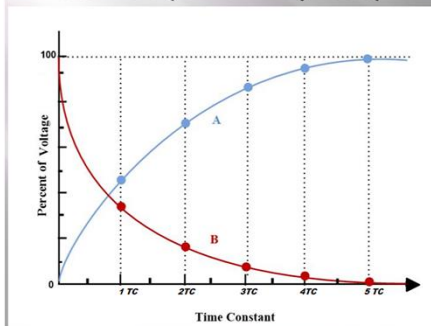
$$V_c = V_s(1 - e^{-t/RC}) = 10(1 - e^{-\frac{1}{1}}) = 10(1 - 0.367) = 10(0.663) = 6.63 \text{ Volts}$$




Time Constant	RC Value	Percentage of Maximum	
		Voltage	Current
0.5 time constant	0.5RC	39.3%	60.7%
0.7 time constant	0.7RC	50.0%	49.7%
1.0 time constant	1RC	63.2%	36.8%
2.0 time constants	2RC	86.5%	13.5%
3.0 time constants	3RC	95.0%	5.0%
4.0 time constants	4RC	98.2%	1.8%
5.0 time constants	5RC	99.3%	0.7%

Al's Electronic Class Room

Capacitance

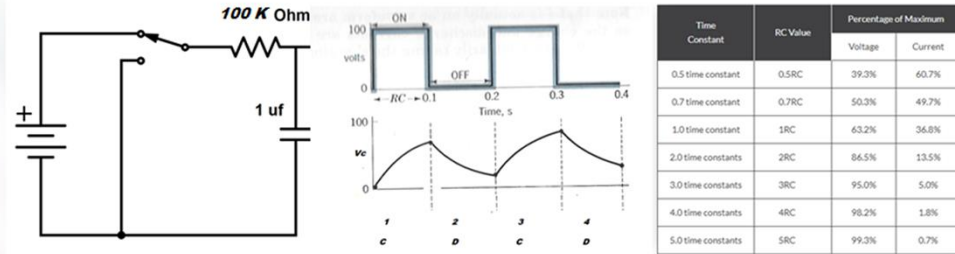Resistor & Capacitor time Constant(s), *RC time constant(s)*



- $TC = R \times C; (100 \times 10^{-3}) \times (1 \times 10^{-6})$
 $TC = 0.1 \text{ Seconds}$


Capacitor

1. $0.632 \times 100 = 63.2 \text{ Volts}$
2. $63.2 - (0.632 \times 63.2) \text{ volts} = 23.23 \text{ Volts}$
3. $((100 - 23.23) \times 0.632) + 23.23 = 71.7 \text{ Volts}$
4. $71.7 - (0.632 \times 71.7) \text{ Volts} = 26.4 \text{ Volts}$

Al's Electronic Class Room

Capacitance

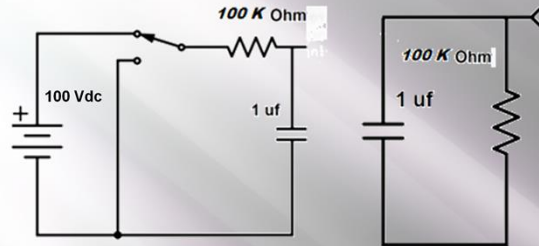Resistor & Capacitor time Constant(s), *RC time constant(s)*



Time Constant	RC Value	Percentage of Maximum	
		Voltage	Current
0.5 time constant	0.5RC	39.3%	60.7%
0.7 time constant	0.7RC	50.3%	49.7%
1.0 time constant	1RC	63.2%	36.8%
2.0 time constants	2RC	86.5%	13.5%
3.0 time constants	3RC	95.0%	5.0%
4.0 time constants	4RC	98.2%	1.8%
5.0 time constants	5RC	99.3%	0.7%

- $TC = R \times C; (100 \times 10^3) \times (1 \times 10^{-6})$
 $TC = 0.1 \text{ Seconds}$


Capacitor

- $0.632 \times 100 = 63.2 \text{ Volts}$
- $63.2 - (0.632 \times 63.2) \text{ volts} = 23.3 \text{ Volts}$
- $((100 - 23.23) \times 0.632) + 23.23 = 71.7 \text{ Volts}$
- $71.7 - (0.632 \times 71.7) \text{ Volts} = 26.4 \text{ Volts}$

Resistor

- $100 \text{ Volts} - 63 \text{ Volts} = 37 \text{ Volts}$
- $100 \text{ Volts} - 23.3 \text{ Volts} = 76.7 \text{ Volts}$
- $100 \text{ volts} - 71.6 \text{ Volts} = 28.4 \text{ Volts}$
- $100 \text{ volts} - 26.5 \text{ Volts} = 73.5 \text{ Volts}$

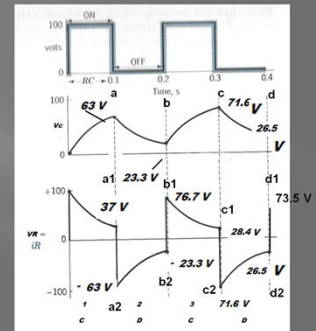
- $37 \text{ Volts} - 100 \text{ Volts} = -63 \text{ Volts}$
- $76.7 \text{ Volts} - 100 \text{ Volts} = -23.3 \text{ Volts}$
- $28.4 \text{ Volts} - 100 \text{ Volts} = -71.6 \text{ Volts}$
- $73.5 \text{ Volts} - 100 \text{ Volts} = -26.5 \text{ Volts}$



Al's Electronic Class Room


Capacitance

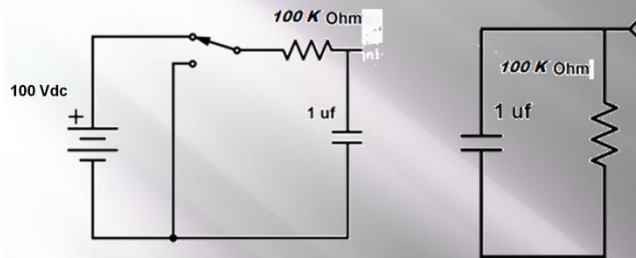Resistor & Capacitor time Constant(s), *RC time constant(s)*



- $TC = R \times C; (100 \times 10^3) \times (1 \times 10^{-6})$
 $TC = 0.1 \text{ Seconds}$


Time Constant	RC Value	Percentage of Maximum	
		Voltage	Current
0.5 time constant	0.5RC	39.3%	60.7%
0.7 time constant	0.7RC	50.3%	49.7%
1.0 time constant	1RC	63.2%	36.8%
2.0 time constants	2RC	86.5%	13.5%
3.0 time constants	3RC	95.0%	5.0%
4.0 time constants	4RC	98.2%	1.8%
5.0 time constants	5RC	99.3%	0.7%

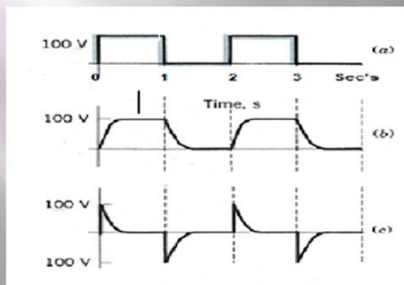

Al's Electronic Class Room


Capacitance

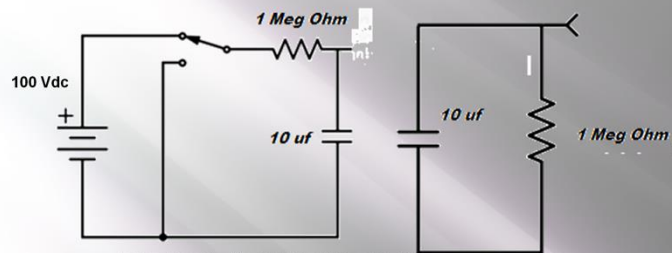Resistor & Capacitor time Constant(s), RC time constant(s)



- $TC = R \times C; (1 \times 10^6) \times (10 \times 10^{-6})$
 $TC = 10 \text{ Seconds}$

Time Constant	RC Value	Percentage of Maximum	
		Voltage	Current
0.5 time constant	0.5RC	39.3%	60.7%
0.7 time constant	0.7RC	50.3%	49.7%
1.0 time constant	1RC	63.2%	36.8%
2.0 time constants	2RC	86.5%	13.5%
3.0 time constants	3RC	95.0%	5.0%
4.0 time constants	4RC	98.2%	1.8%
5.0 time constants	5RC	99.3%	0.7%

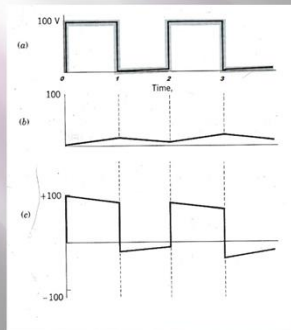

$$VC = VS(1 - e^{-t/RC})$$

Al's Electronic Class Room

Al's Electronic Class Room

