


TEACHERS: VANKOOKZ

2023




### DI DI MASTER CLASS

# 12 VOLT SYSTEM PHASE 5 WIRING 101

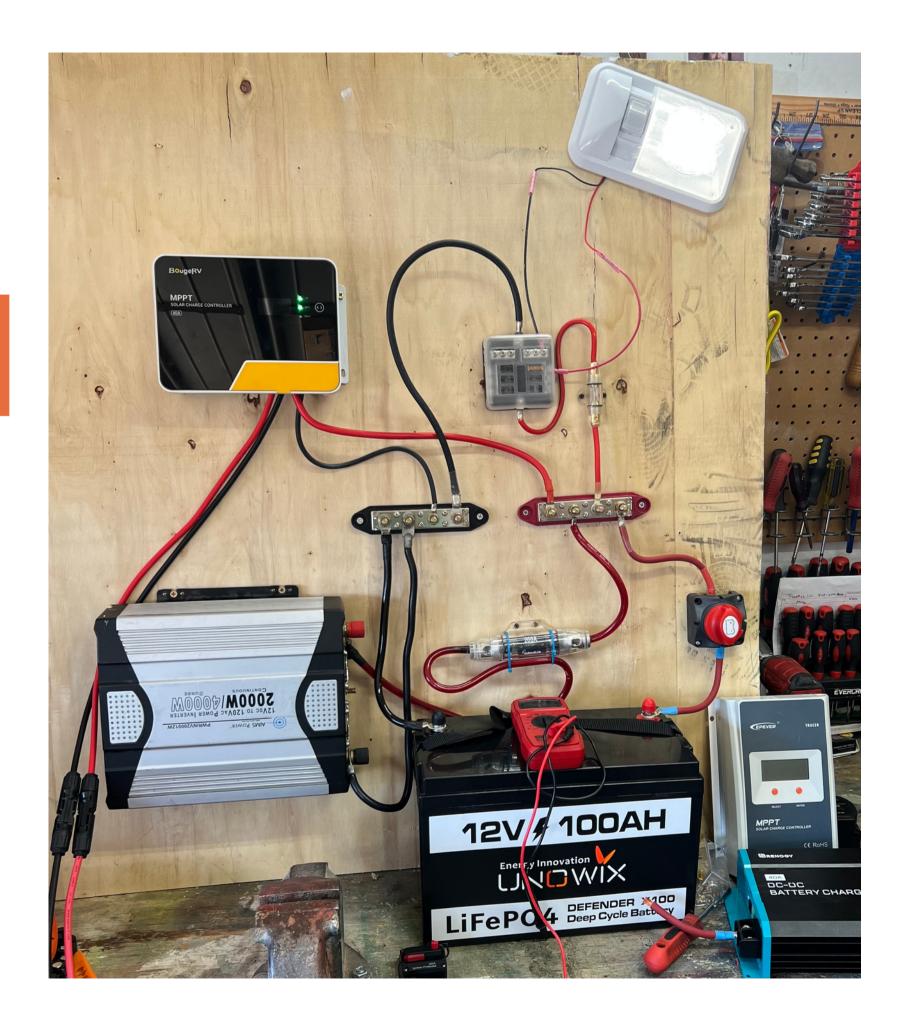





## WIRING BATTERIES IN PARALLEL

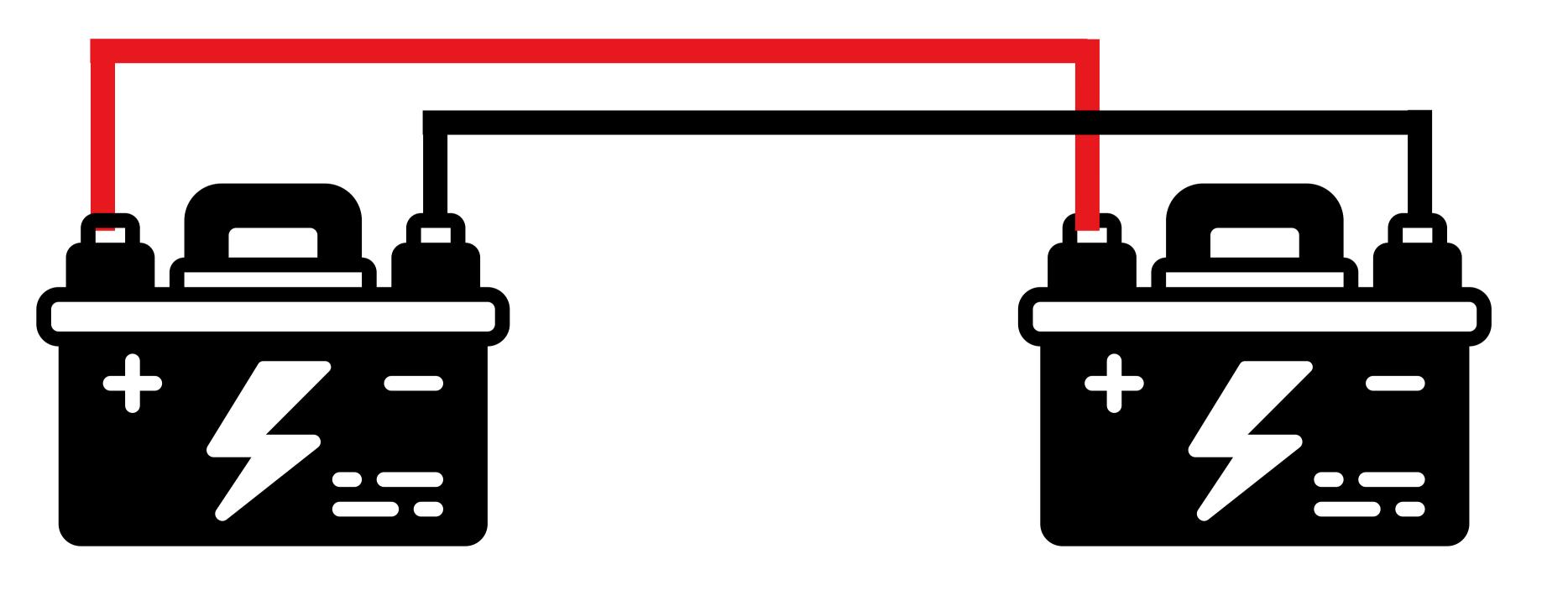

#### GROUNDING YOUR BATTERY BANK

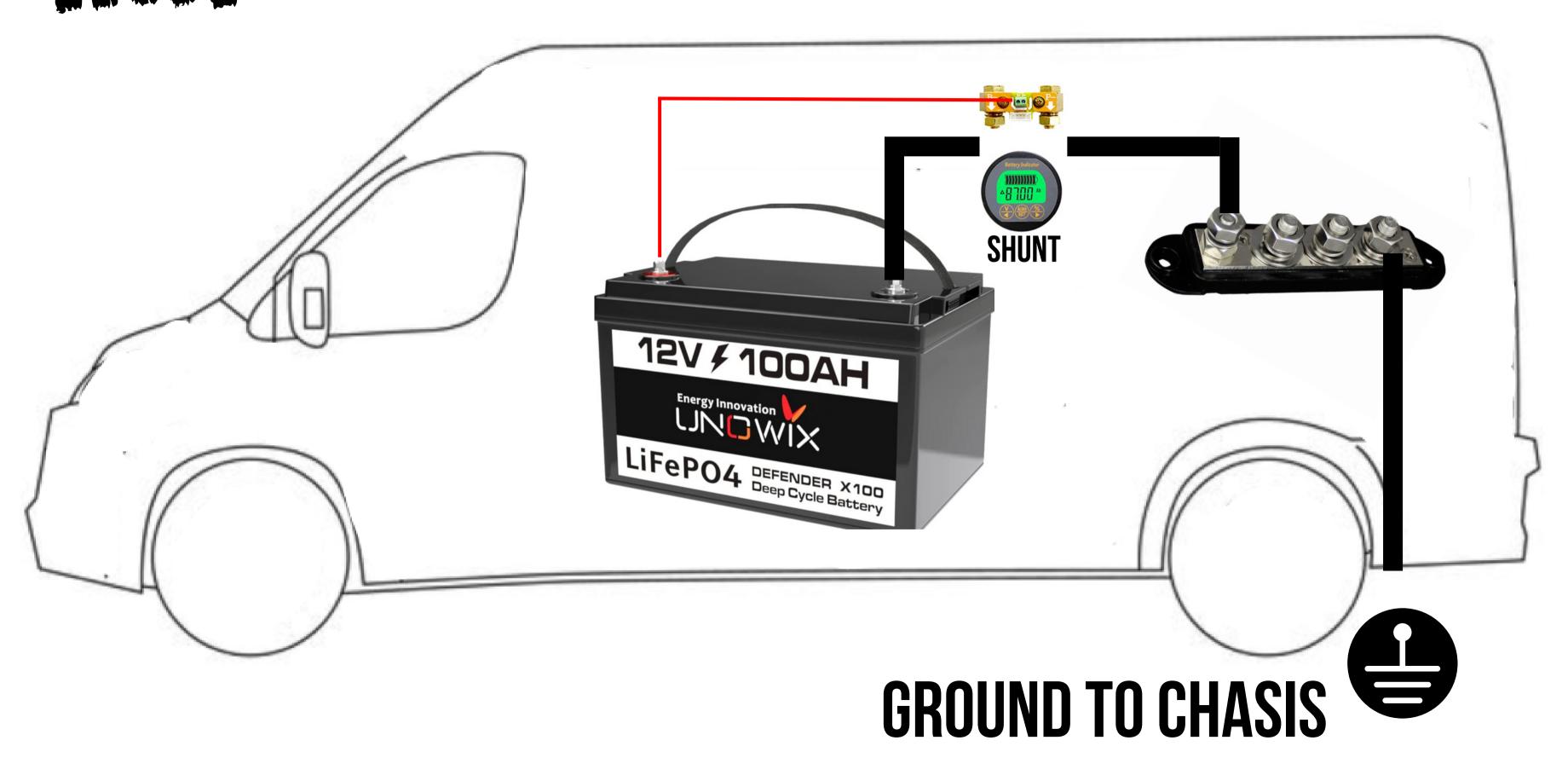



#### INSTALLING BUS BARS DIAGRAM

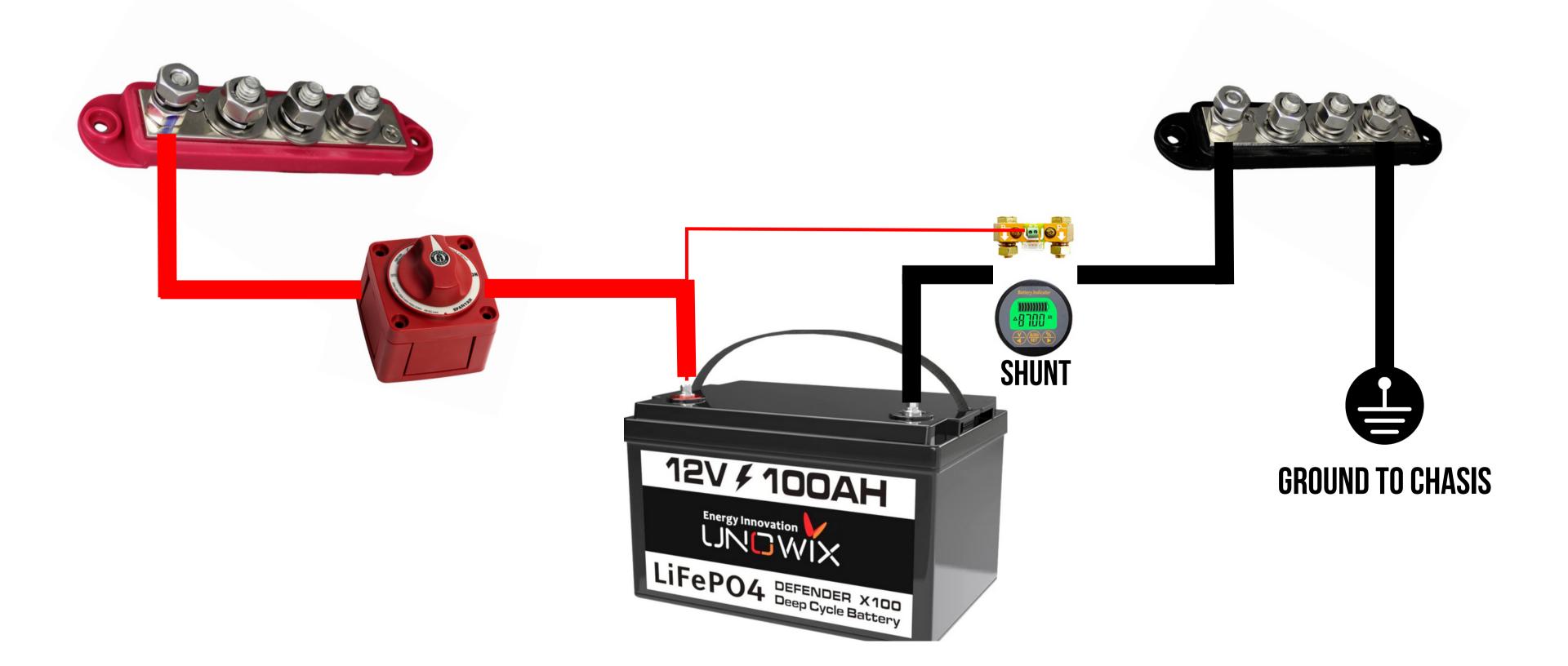





#### **LOAD**

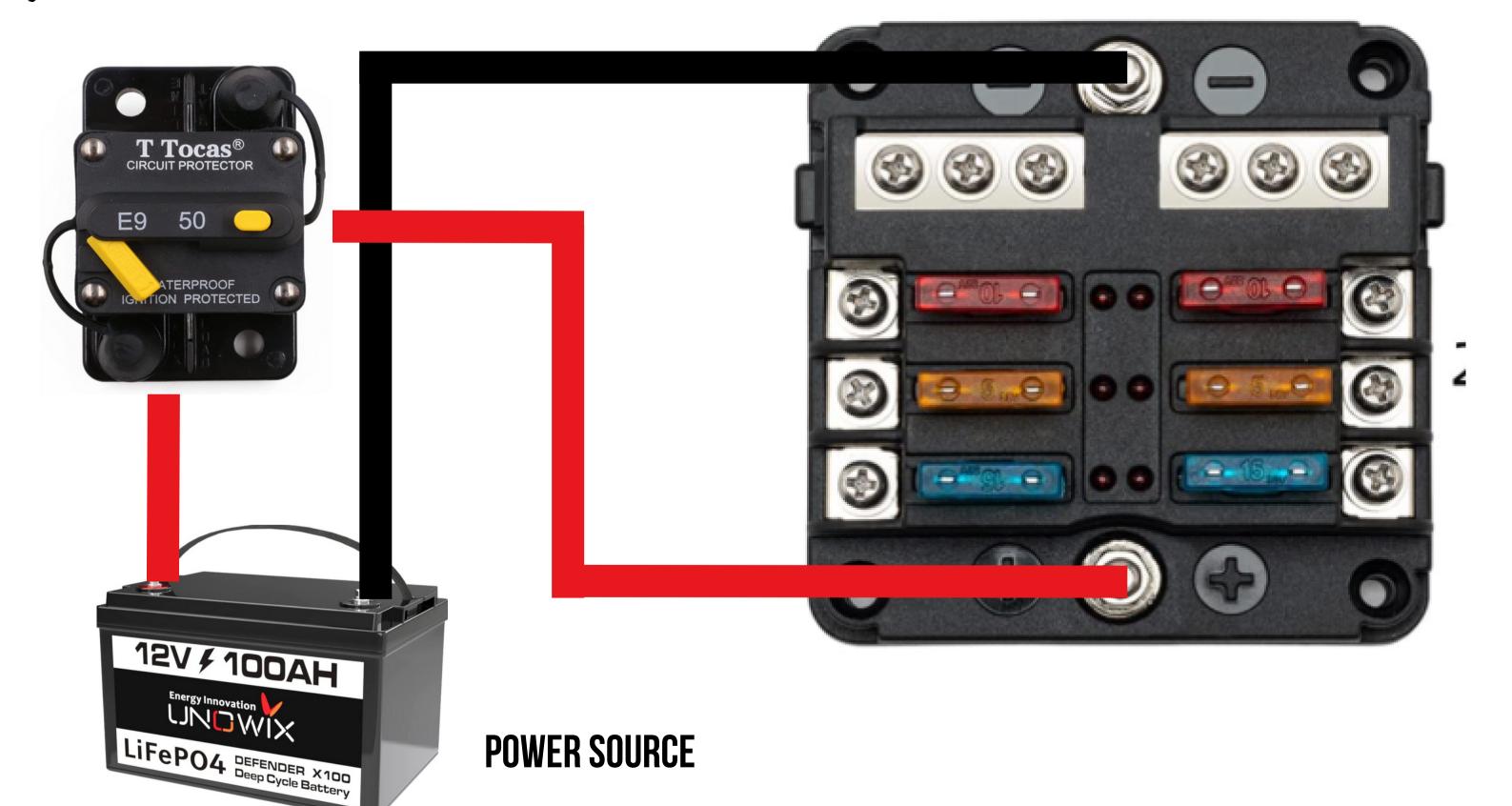


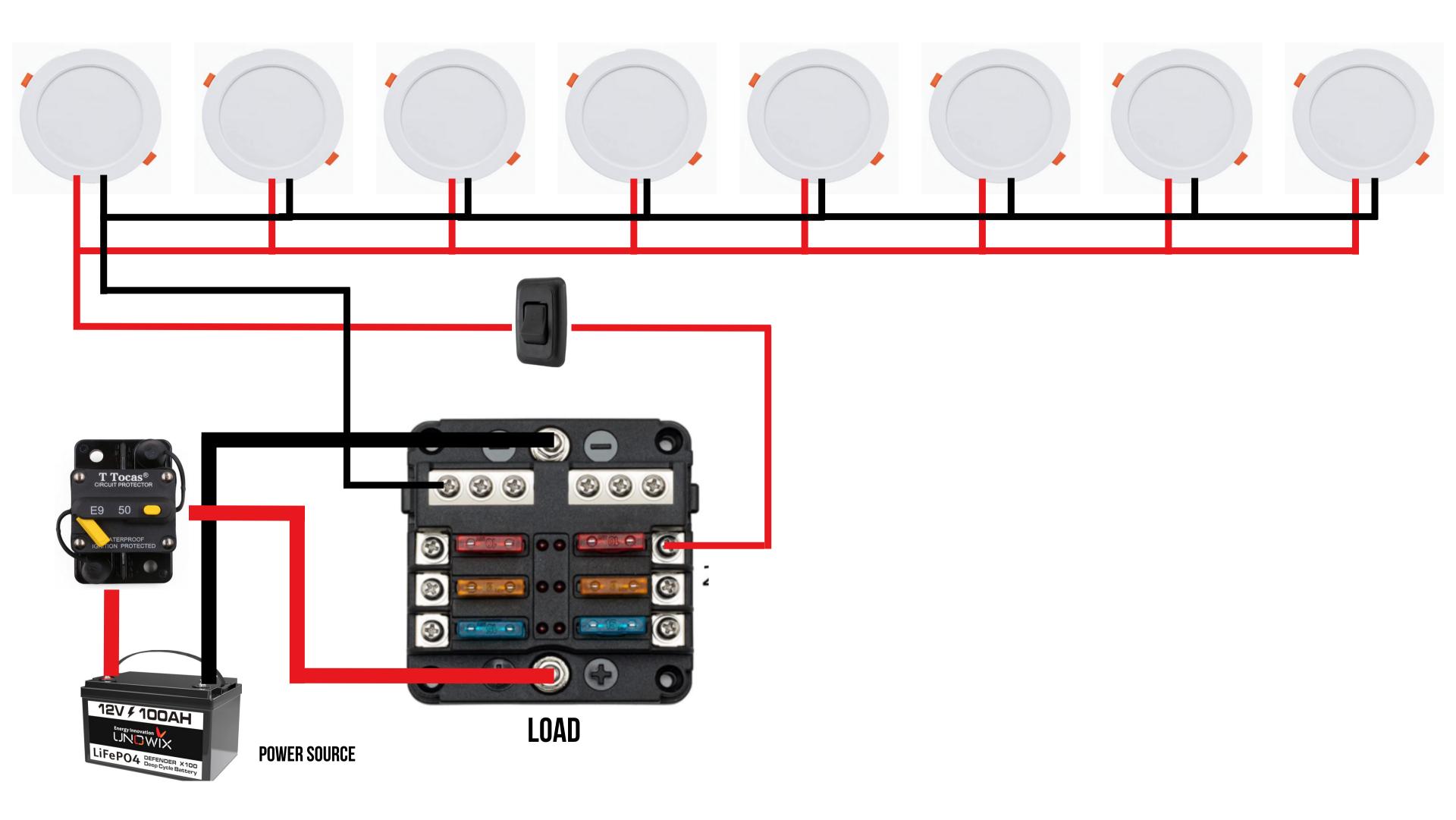


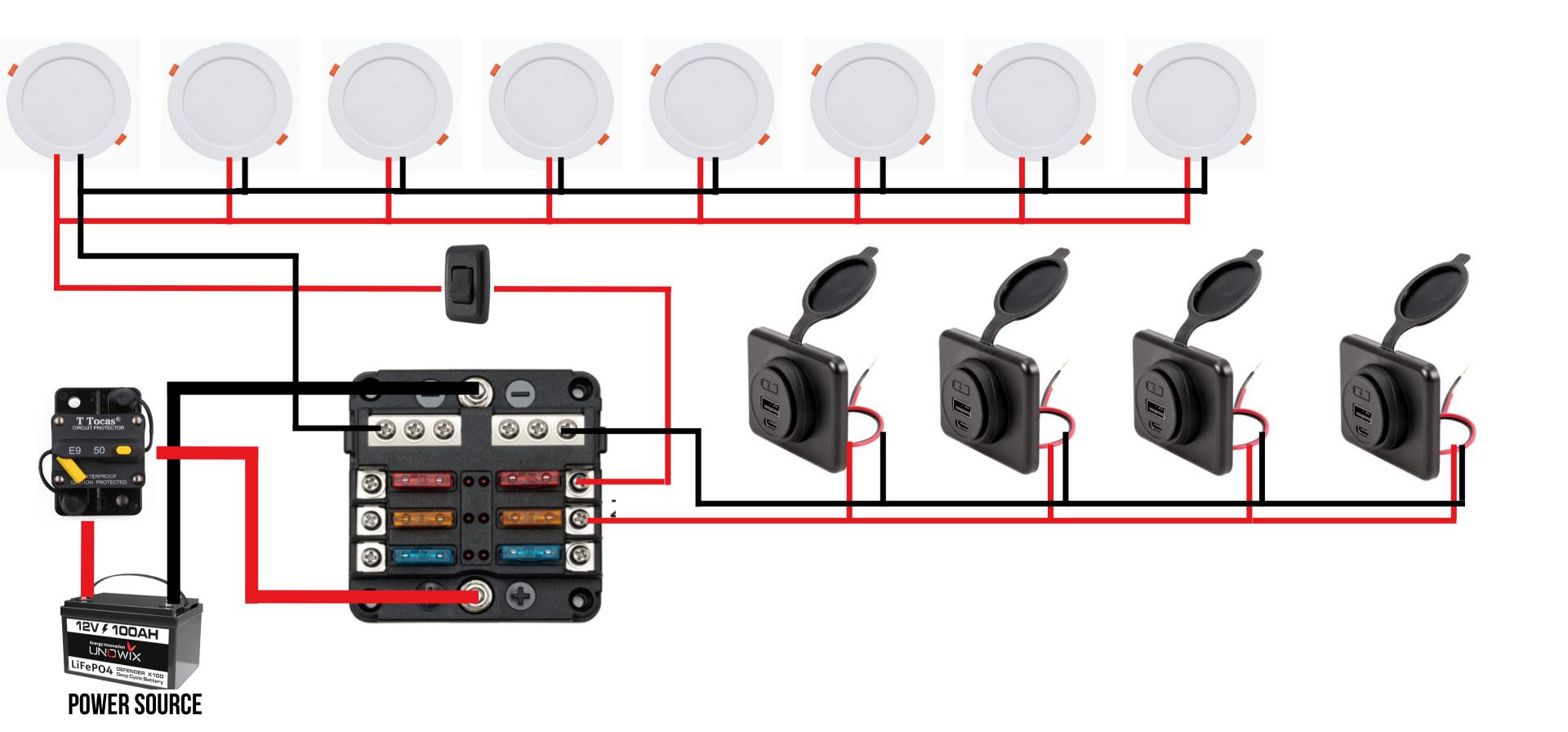

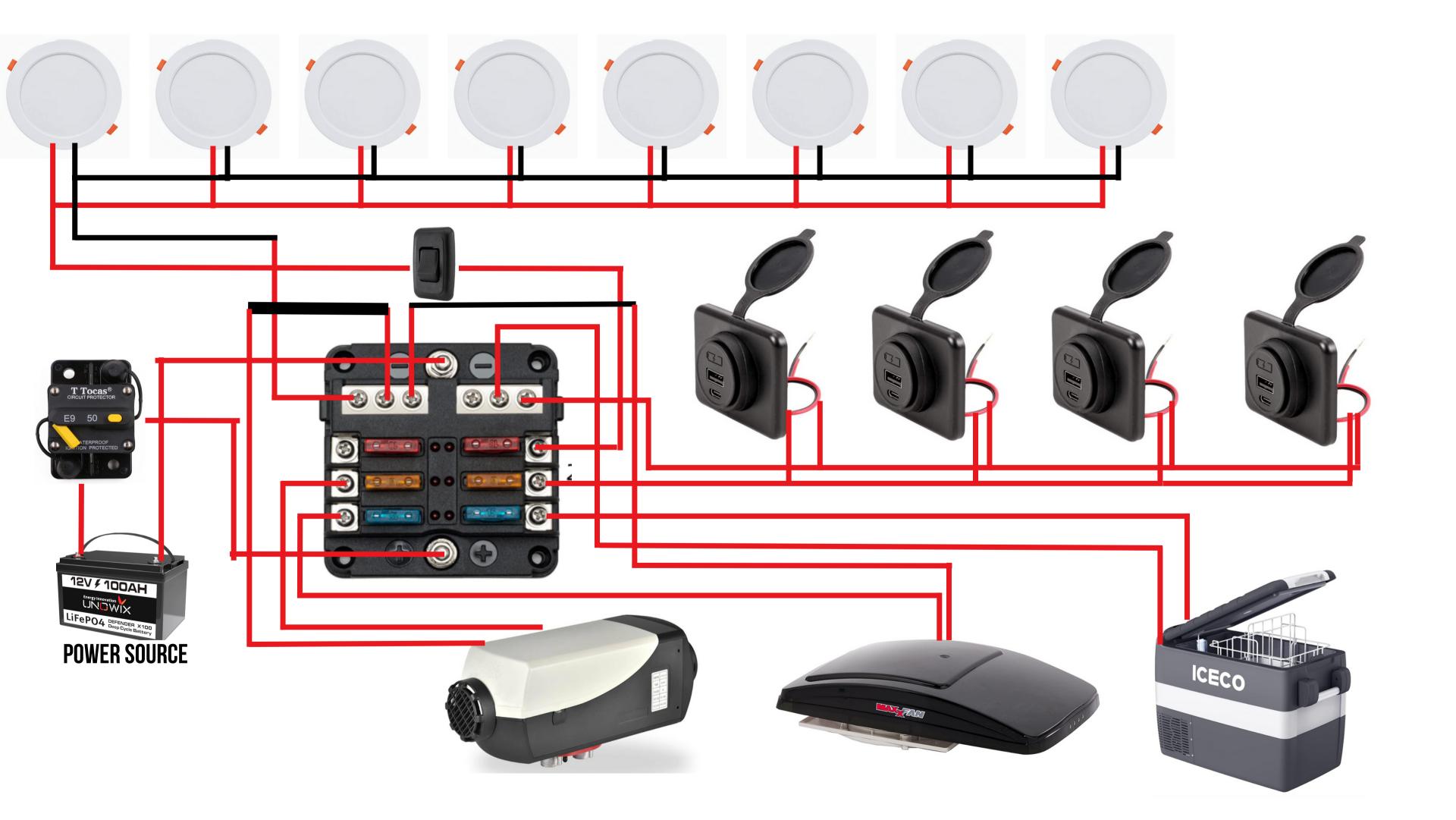



### WING A CHARGE CONTROLLER

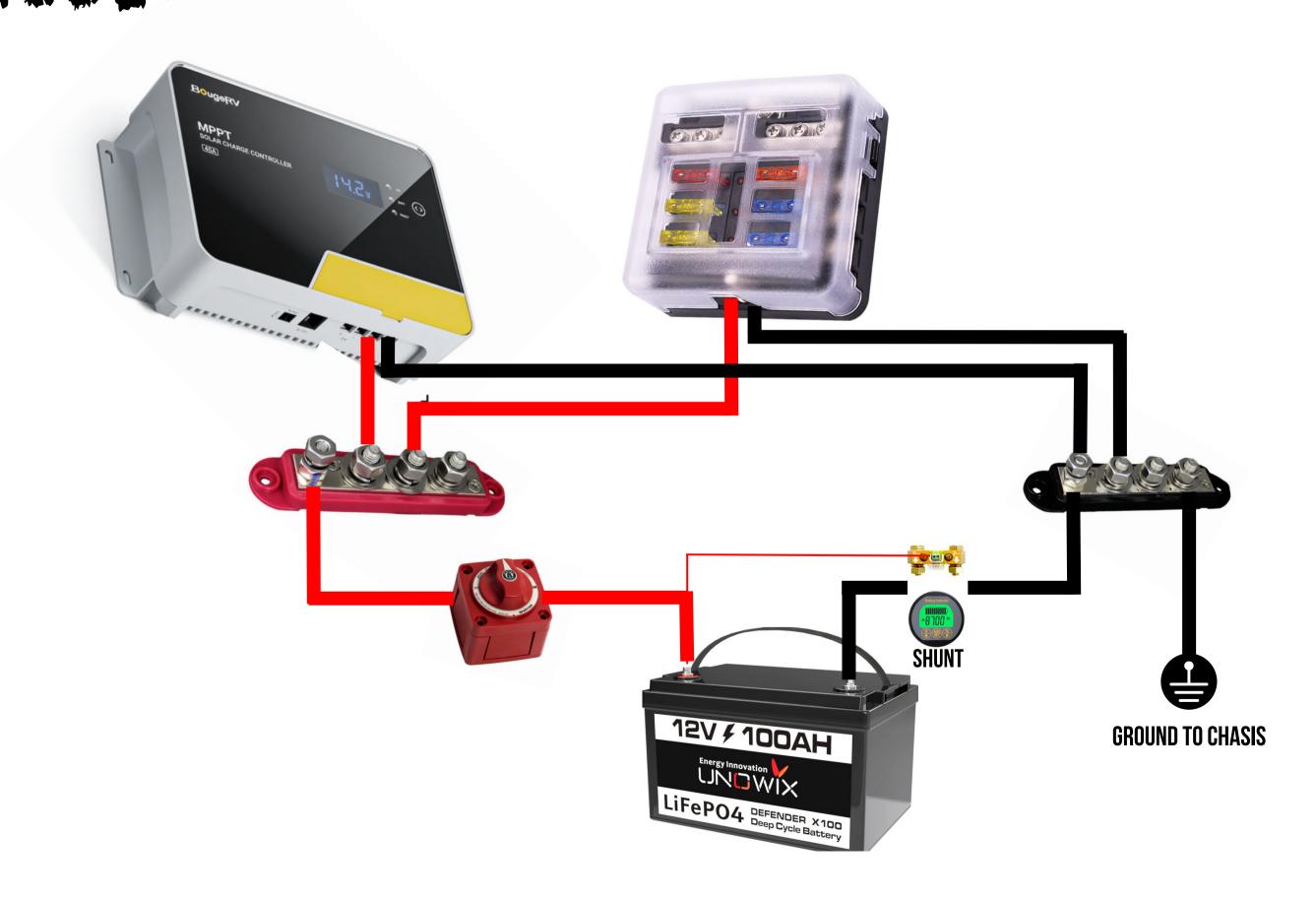

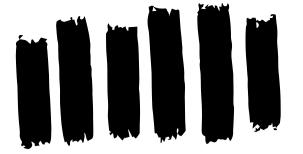

#### WING A CHARGE CONTROLLER

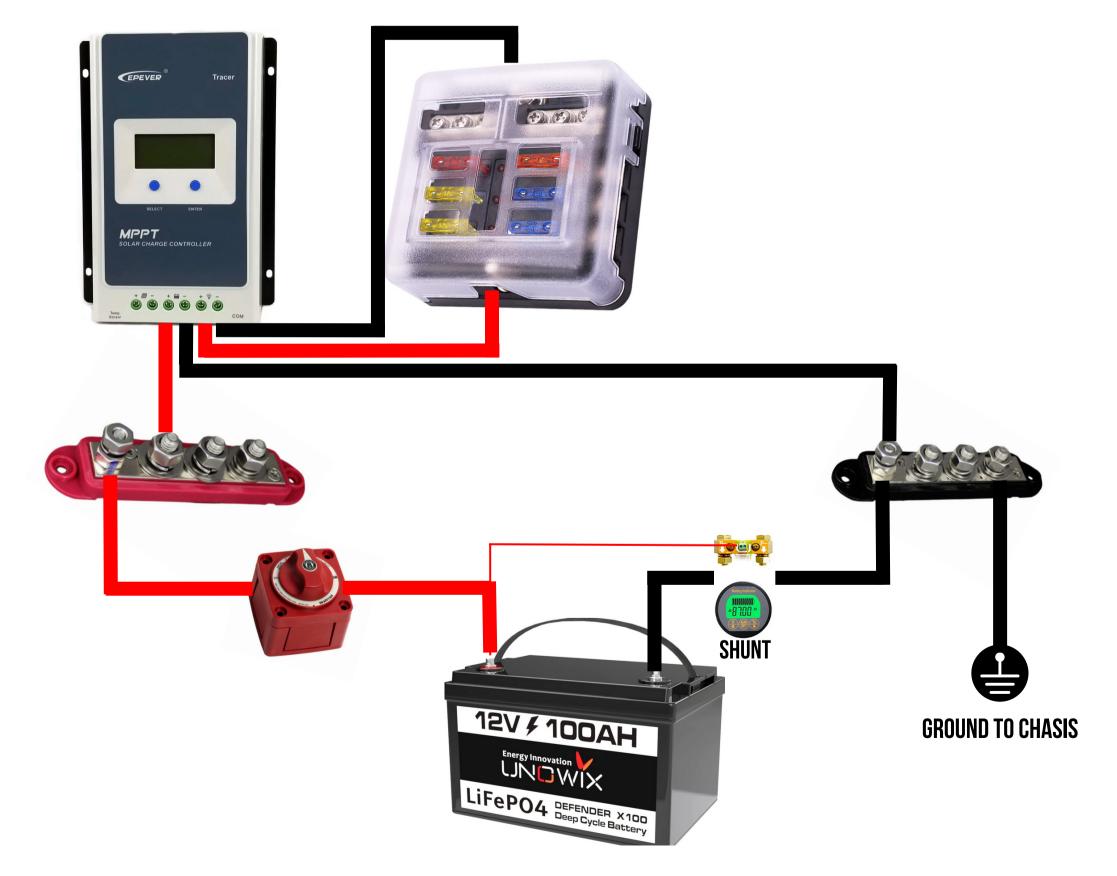


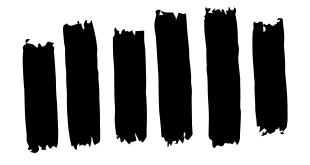


#### WIRING A CHARGE CONTROLLER



#### BASIC 12 VOLT WIRING DIAGRAM

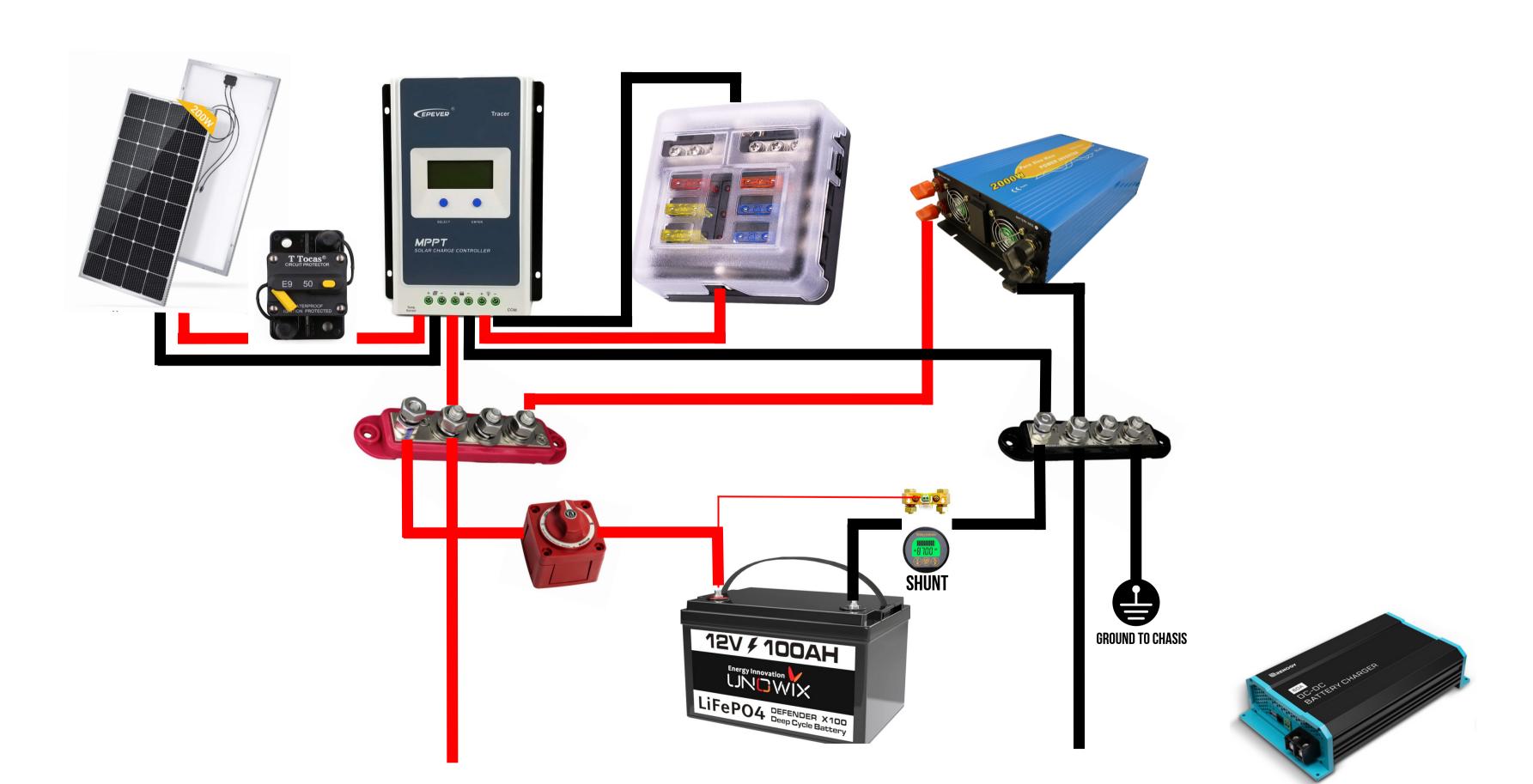


#### THE DC TO DC CHARGER DIAGRAM

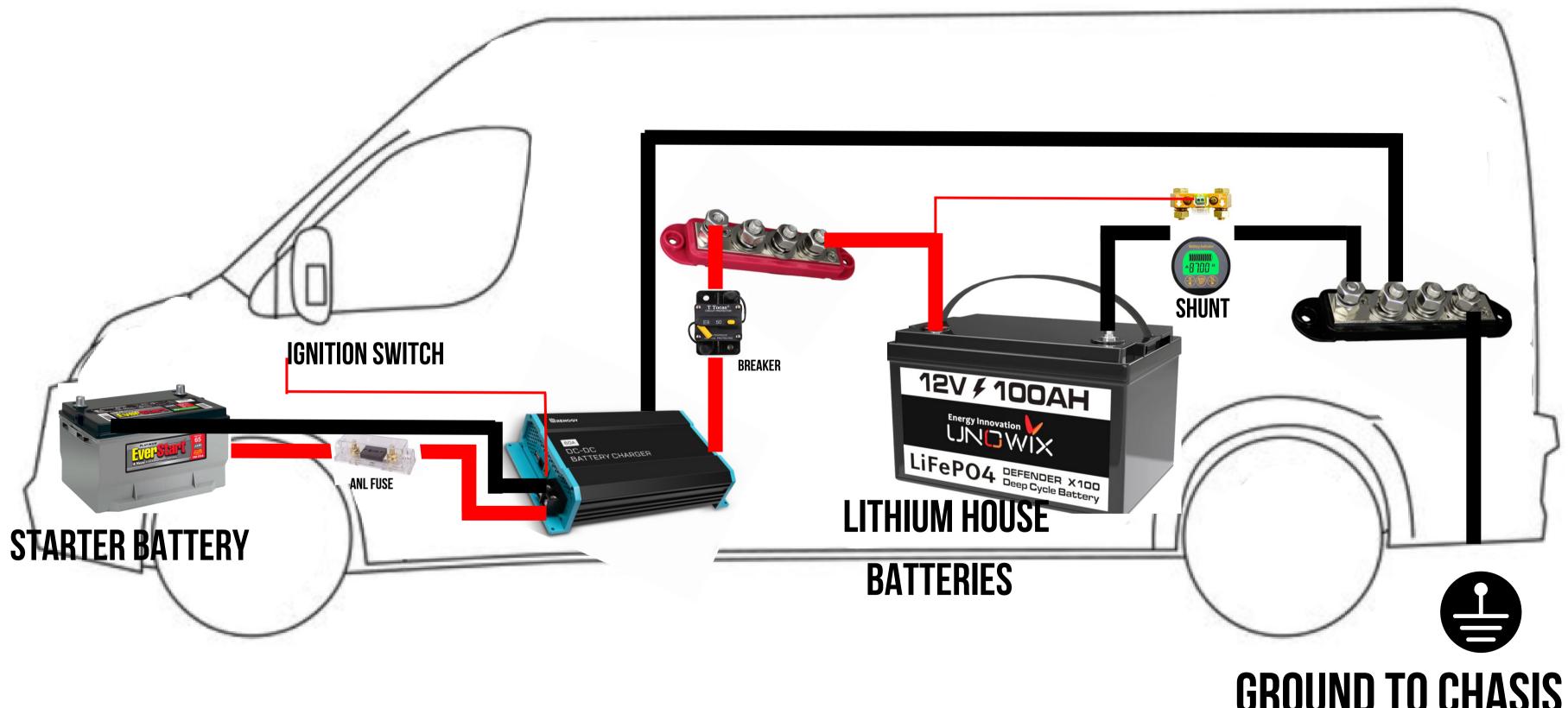

**GROUND TO CHASIS** 

#### THE BATTERY ISOLATOR DIAGRAM

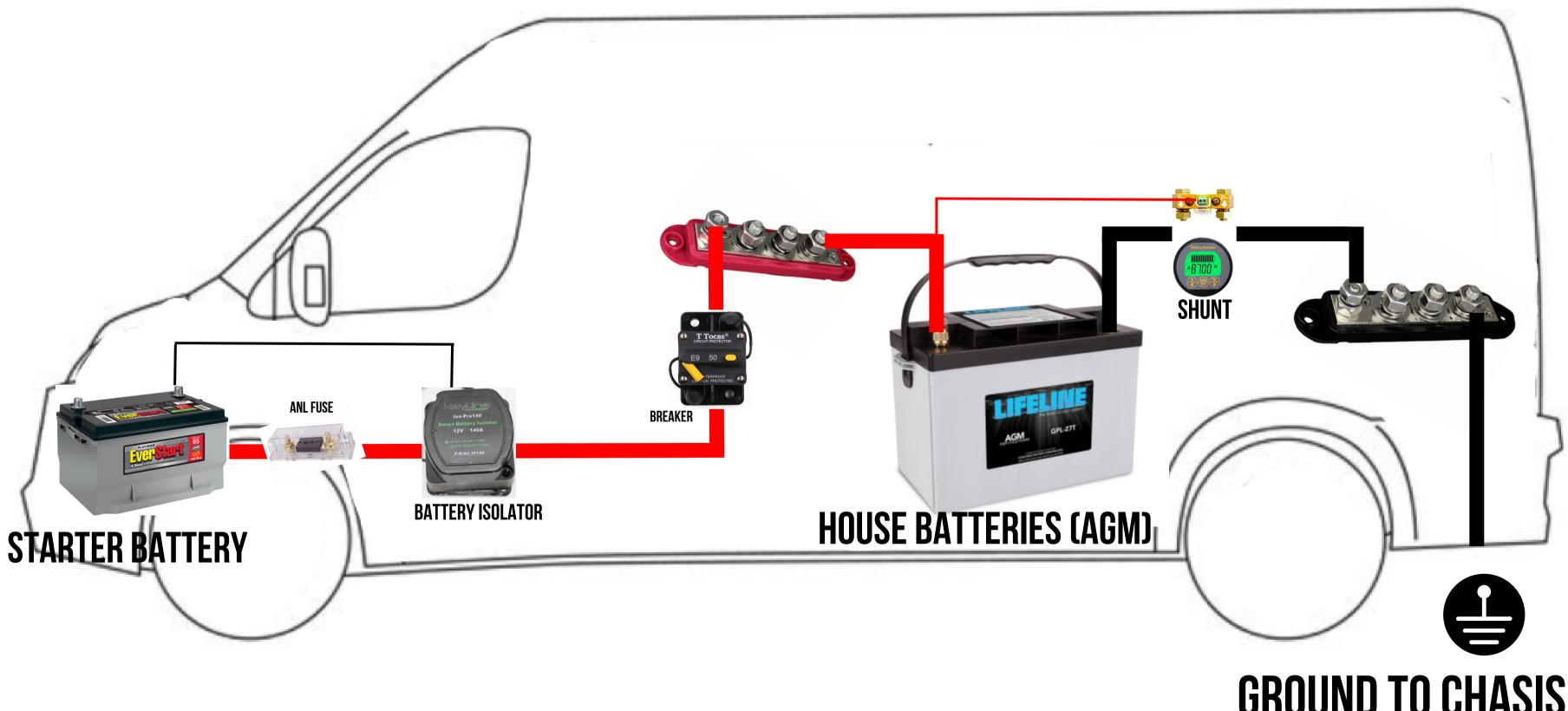

**GROUND TO CHASIS** 



TEACHERS: VANKOOKZ 2022



###