
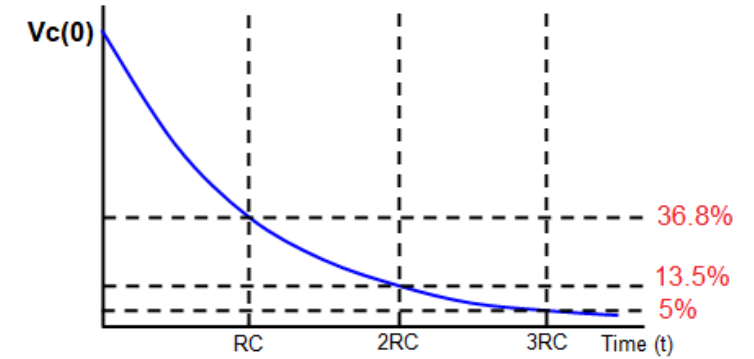
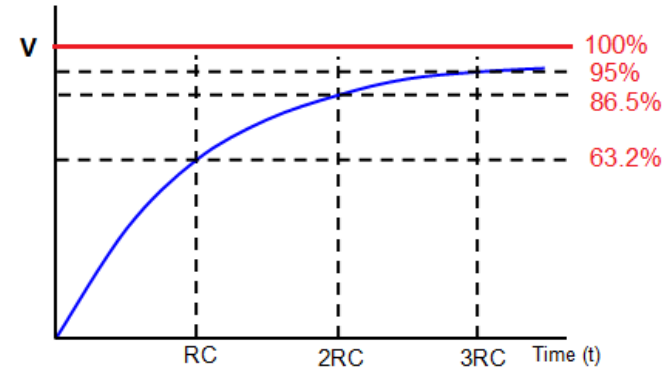


# RC Transient response

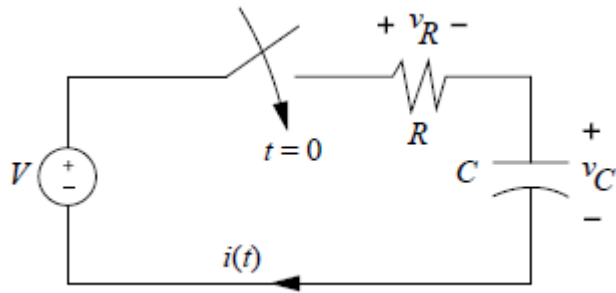

Time  $t \geq 0$  Initial voltage across capacitor –  $v_c(0)$  Time constant  $\tau = RC$  Applied Voltage =  $V$

$$v_c(t) = v_c(0)e^{-\frac{t}{RC}} + V(1 - e^{-\frac{t}{RC}})$$

$$i(t) = \frac{[V - v_c(0)]}{R} e^{-t/RC}$$



$$v_R(t) = i(t)R = [V - v_c(0)]e^{-t/RC}$$

| Time constant $\tau = RC$ | % charged | % discharged |
|---------------------------|-----------|--------------|
| 1                         | 63.2%     | 36.8%        |
| 2                         | 86.5%     | 13.5%        |
| 3                         | 95%       | 5%           |
| 4                         | 98.2%     | 1.8%         |
| 5                         | 99.3%     | 0.7%         |

# RC Transient response



STUDY FOR FE

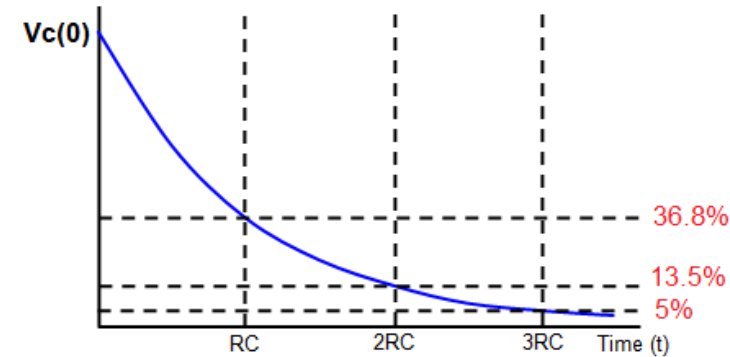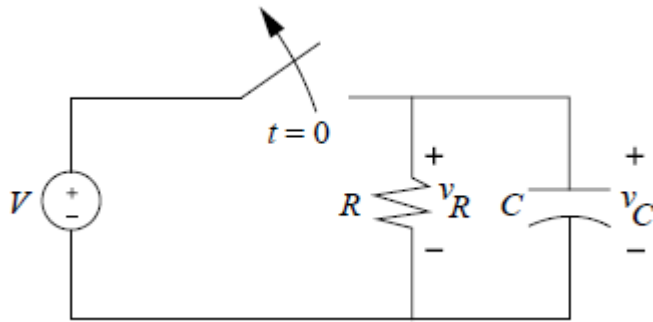

Time  $t \geq 0$  Initial voltage across capacitor –  $v_c(0)$  Time constant  $\tau = RC$  Applied Voltage =  $V$

$$v_c(t) = v_R(t) = V e^{-\frac{t}{RC}}$$

$$i_R(t) = -i_C(t) = \frac{V}{R} e^{-t/RC}$$

| Time constant $\tau = RC$ | % charge remaining |
|---------------------------|--------------------|
| 1                         | 36.8%              |
| 2                         | 13.5%              |
| 3                         | 5%                 |
| 4                         | 1.8%               |
| 5                         | 0.7%               |