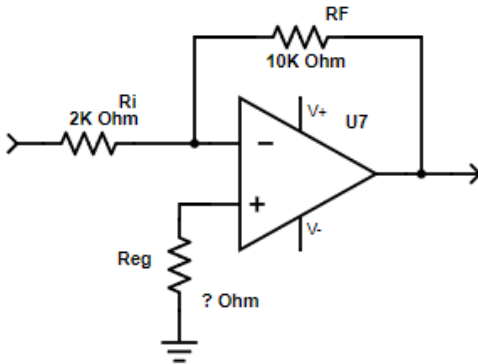



Electronic Al's Class Room

www.alselectronicclassroom.com



From the circuit on the left Find the following

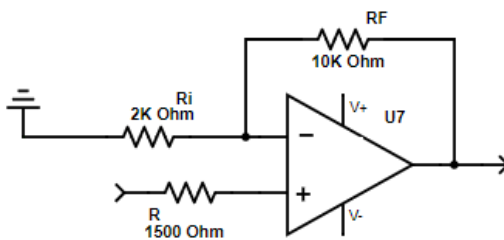- Gain of the Amplifier: $a_v = 5$
- Value of Reg. 1.666 K Ohm
- $2\text{ v P-P Sinewave In}$ What is the Output 10 v P-P
- Are the input and Output in Phase or out of Phase ; Out of Phase




From the circuit on the left Find the following

- Gain of the Amplifier: $a_v = 6$
- $2\text{ v P-P Sinewave In}$ What is the Output 12 P-P
- Are the input and Output in Phase or out of Phase; In Phase

Electronic Al's Class Room

www.alselectronicclassroom.com

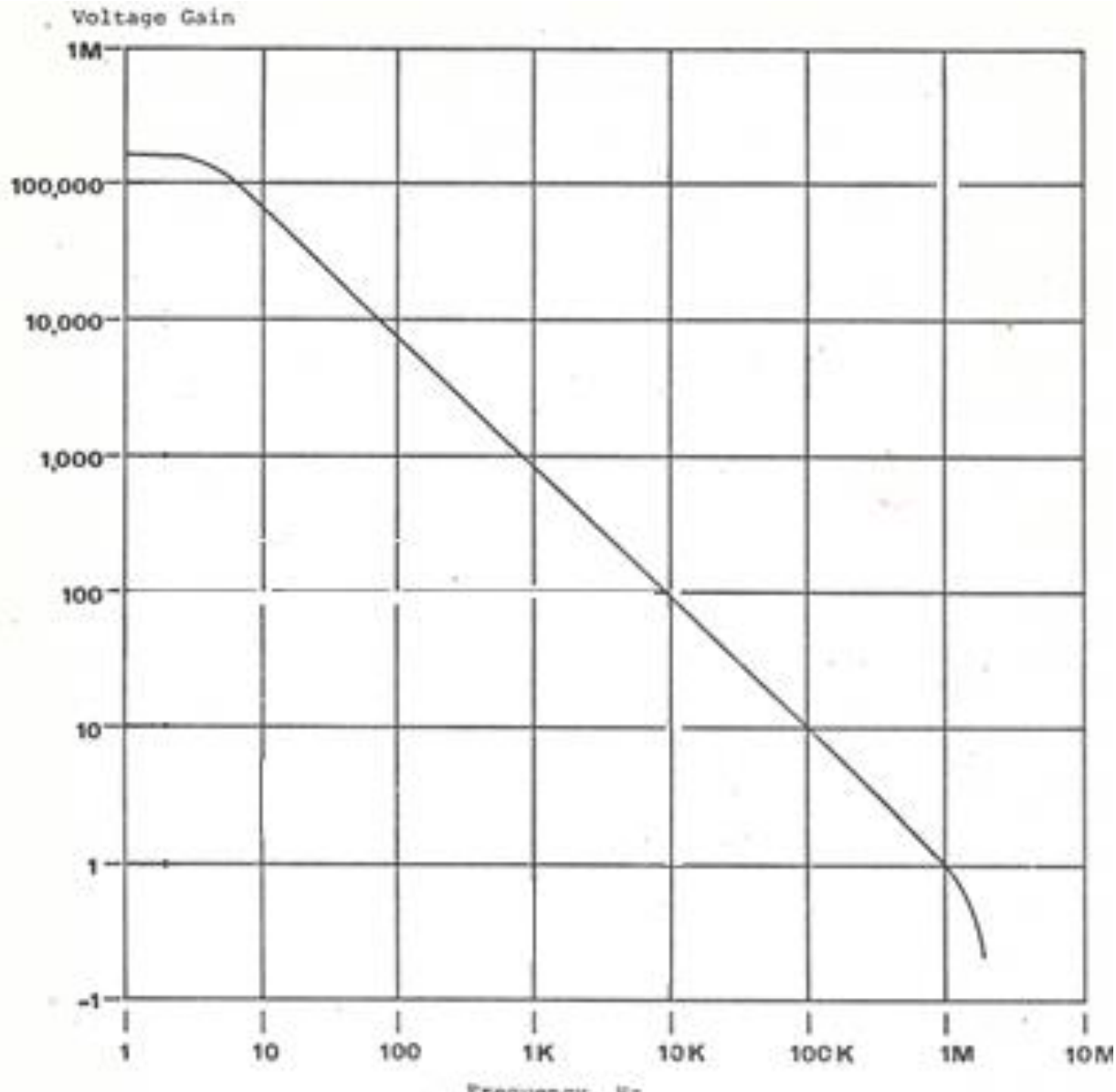


From the Graph above : Circuit designer has designed a circuit that has gain of 50 he believe's that operational amplifier with a constant gain to a frequency 100 KHz. Will this work using the graph at top? No

If not what is the frequency? 50 KHz

Electronic Al's Class Room

www.alselectronicclassroom.com

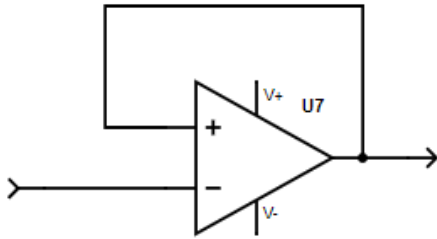

From the circuit on the left Find the following

- Gain of the Amplifier 1
- 2 v P-P Sinewave In What is the Output 2v P-P
- Are the input and Output in Phase or out of Phase ; In Phase