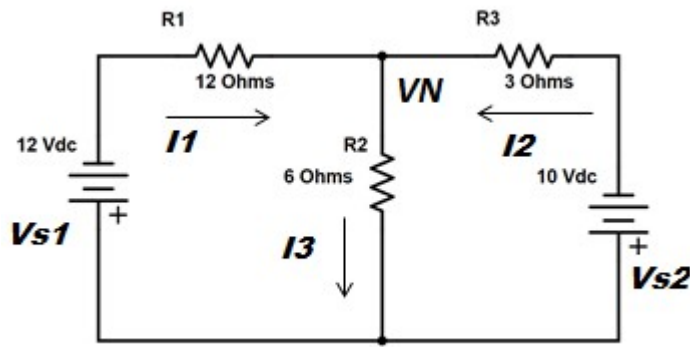
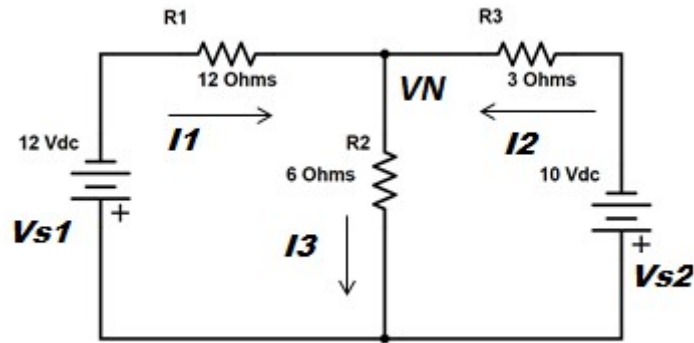


Find V_n using Kirchoffs Voltage Analysis



Find: V_n , V_{R1} , V_{R3} & $I1$ & $I2$ & $I3$

Find V_n using Kirchoffs Voltage Analysis



$$1. I_1 + I_2 = I_3$$

$$2. V_{R1}/R_1 + V_{R3}/V_n = V_n/R_3 \quad (I \text{ in terms of } V/R)$$

$$3. V_{R1} + V_n = 12 \text{ Vdc} \quad \text{or} \quad V_{R1} = 12 \text{ Vdc} - V_n \quad (V_{s1} \text{ in terms of } V_{s1} \text{ \& } V_n)$$

$$V_{R3} + V_n = 10 \text{ Vdc} \quad \text{or} \quad V_{R3} = 10 \text{ Vdc} - V_n \quad (V_{s2} \text{ in terms of } V_{s2} \text{ \& } V_n)$$

$$4. (12 - V_n/12) + (10 - V_n/3) = V_n/6 \quad \text{Divide by 12}$$

$$5. -V_n + 4(10 - V_n) = 2V_n$$

$$6. -2 V_n + 40 = 2 V_n$$

$$7. 40 = 4 V_n$$

$$8. V_n = 10$$

Check

$$V_{R1} = 12 \text{ vdc} - V_n ; 12 \text{ vdc} - 10 \text{ Vdc} = 2 \text{ Vdc}$$

$$V_{R3} = 10 \text{ Vdc} - 10 \text{ vdc} = 0 \text{ vdc}$$

$$V_{s1} = V_n + V_{R1}; 10 \text{ Vdc} + 2 \text{ Vdc} = 12 \text{ Vdc}$$

$$V_{s2} = V_n + V_{R3}; 10 \text{ Vdc} + 0 \text{ Vdc} = 10 \text{ Vdc}$$

$$V_{s1} + V_{R1} + V_{R3} + V_{s2} = 0 ; 12 \text{ Vdc} + (-2 \text{ Vdc}) + 0 \text{ Vdc} + -10 \text{ Vdc} = 0$$