

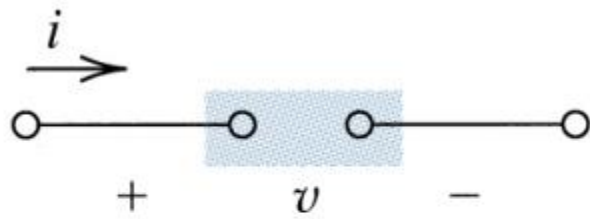


Ideal Diode


NCEES® FE Reference Handbook Page # 384

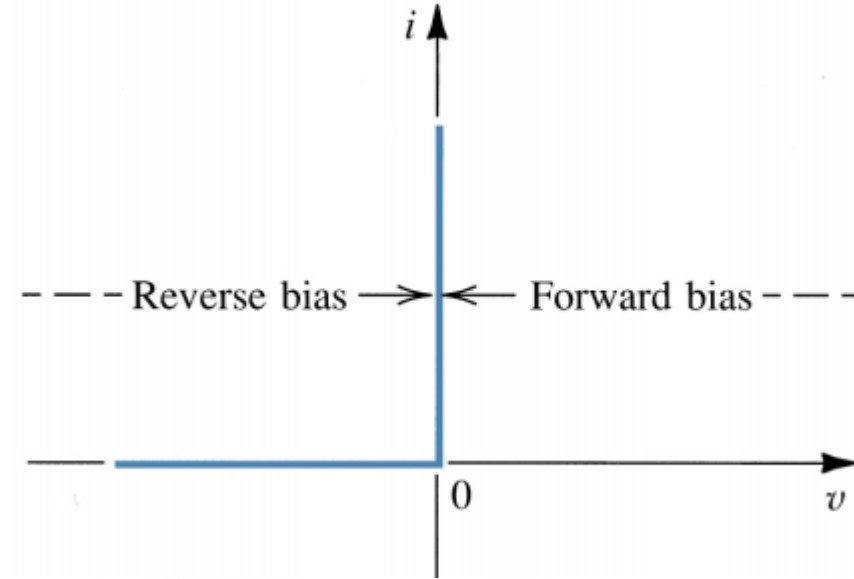

STUDY FOR FE

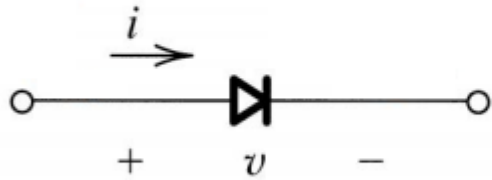

$$v < 0, i = 0$$

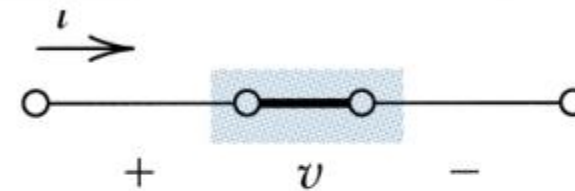

$$v = 0, i > 0$$