

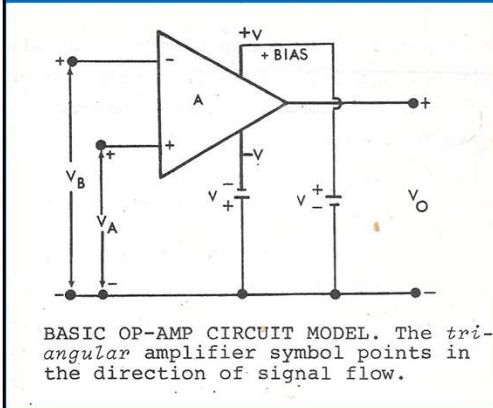
# The Greatest Operational Amplifier Course on the Internet.




Al's Electronic Class Room  
[www.alselectronicclassroom.com](http://www.alselectronicclassroom.com)




- **Operational Amplifier or OP-Amp**
- **There are three basic Operational Configurations**
  - **Inverting**
  - **Non-Inverting**
  - **Differential**
- **We will be discussing the Linear Operational Amplifier First**



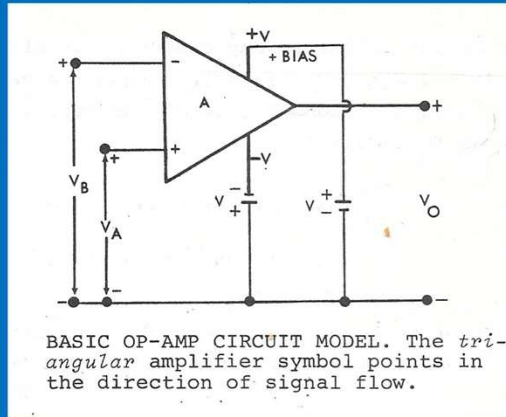- Standard Operational Symbol
- Two Inputs , - Inverting  
+ Non\_Inverting
- Output is taken at the Single Output and  $V_o$  to Gnd.
- The Operational Amplifier has Two Voltage Sources. +V & -V
- $V_o = A(V_A - V_B)$  (Where A is open loop Gain of the Operational Amplifier ) (Op-Amp)
- Typical Open Loop Gain is around 50000.



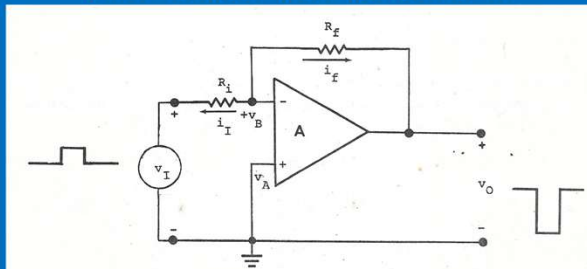- Output of the Operational Amplifier , Cannot have an output greater then either of the Supply Voltage Sources .  $+V$  &  $-V$  .
- Since the typical voltage supply Voltage for the Op - Amp is  $\pm 15$  Volts DC  
Therefore  $(0.3 \text{ M Volts}) \times 50000 = 15 \text{ VDC}$  ; Small input Voltage will hit the rail of the Power supply.




**INVERTING AMPLIFIER.** The feedback resistor  $R_f$  provides a negative-feedback loop from the output to the inverting input. The inverting amplifier has a closed-loop gain equal to  $-(R_f/R_i)$ , where the negative sign indicates that the amplified signal is inverted. The input impedance is equal to the input resistance  $R_i$ .

$V_A$  &  $V_B$  inputs track . Since  $i_i = i_f$  , then  $V_{in} = i_i \times R_i$  ;  $V_{out} = i_f \times R_f$

Close loop Gain  $V_{out} = (V_{in}) \times - \left( \frac{R_f}{R_i} \right)$  ; Input Impedance is  $R_i$

### Inverting Amplifier

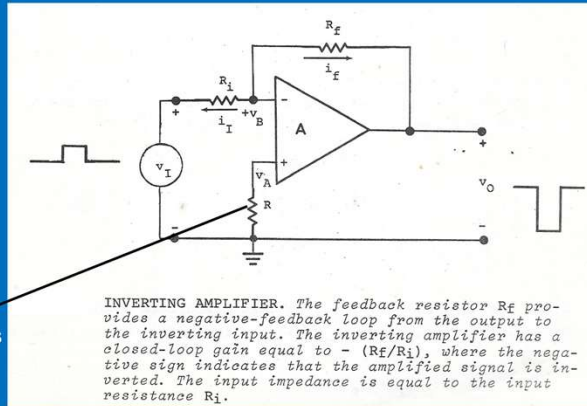


$R = R_f // R_i$   
Balance the Inputs

VA & VB inputs track . Since  $i_i = i_f$  ; then  $V_{in} = i_i \times R_i$  ;  $V_{out} = i_f \times R_f$

Close loop Gain  $V_{out} = (V_{in}) \times - \left( \frac{R_f}{R_i} \right)$  ; Input Impedance is  $R_i$

### Inverting Amplifier

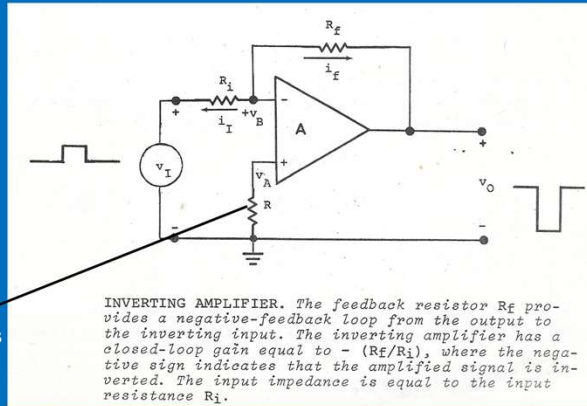


$R = R_f // R_i$   
Balance the Inputs

VA & VB inputs track . Since  $i_i = i_r$  ; then  $V_{in} = i_i \times R_i$  ;  $V_{out} = i_r \times R_f$

Close loop Gain  $V_{out} = (V_{in}) \times - \left( \frac{R_f}{R_i} \right)$  ; Input Impedance is  $R_i$



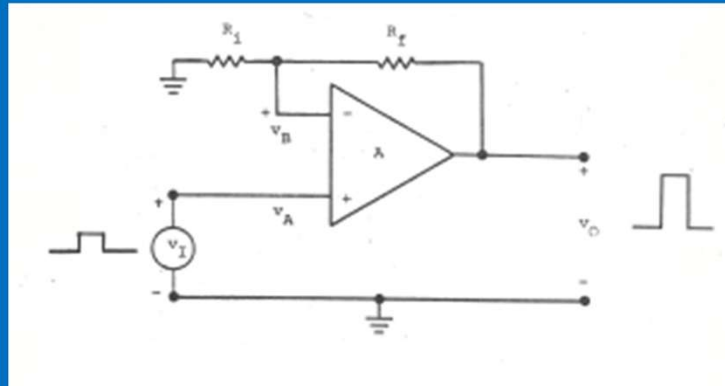
AI's Electronic Class Room  
www.alselectronicclassroom.com  
Non-Inverting Amplifier



- High Input impedance
- Input is in Phase with Output
- Gain is  $1 + \frac{R_f}{R_i} = \text{Output}$
- Also Called a Voltage Follower
- Low Output Impedance
- Primary used a buffer Circuit

AI's Electronic Class Room  
www.alselectronicclassroom.com

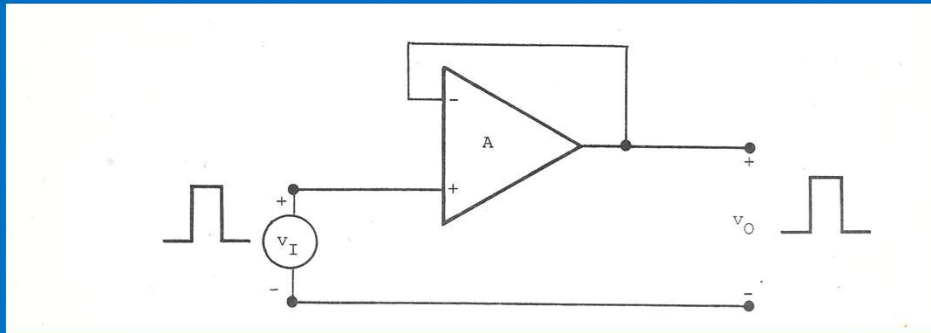
AI's Electronic Class Room  
www.alselectronicclassroom.com  
Unity Gain Voltage Follower



- High Input impedance
- Input is in Phase with Output
- Gain is unity  $V_i = V_o$
- High Input Impedance
- Low Output Impedance
- Primary used as a buffer Circuit

AI's Electronic Class Room  
www.alselectronicclassroom.com


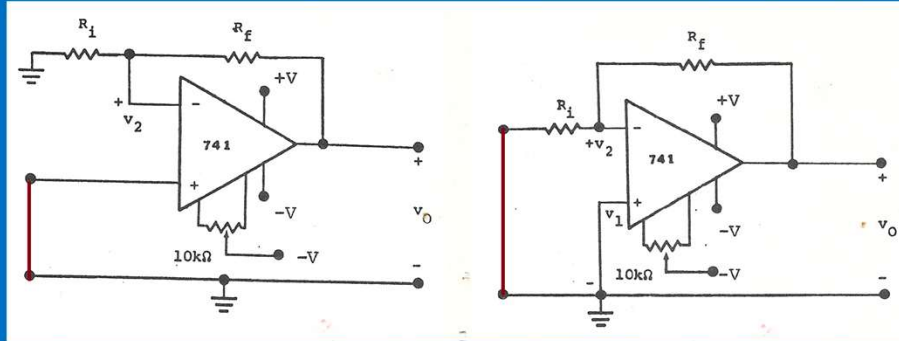
Al's Electronic Class Room  
www.alselectronicclassroom.com  
Off-Set Voltage



- Offset Voltage is caused by the mismatch of internal component's
- Offset voltage is multiplied by the gain therefore if the gain is 10 , the input offset voltage is 10 mv then output offset voltage is 100 mv.
- Potentiometer is placed accross the Null inputs and adjusted out with the Input(s) at ground.


Al's Electronic Class Room  
www.alselectronicclassroom.com

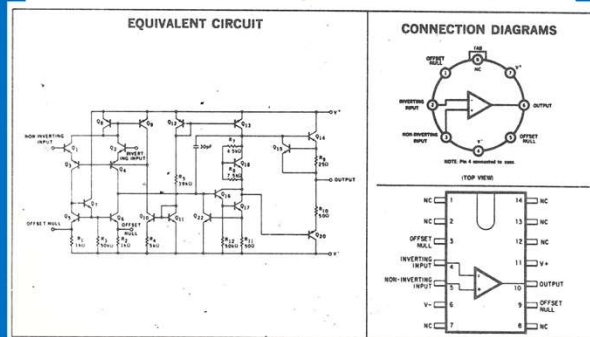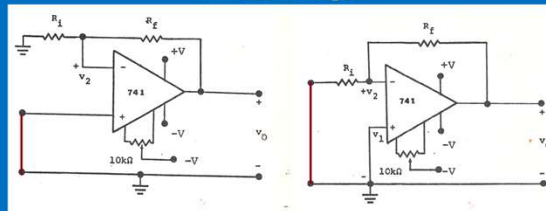Al's Electronic Class Room  
[www.alselectronicclassroom.com](http://www.alselectronicclassroom.com)  
 Off-Set Voltage



Al's Electronic Class Room  
[www.alselectronicclassroom.com](http://www.alselectronicclassroom.com)

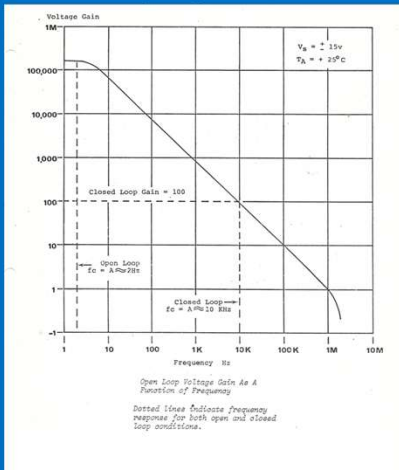Al's Electronic Class Room  
[www.alselectronicclassroom.com](http://www.alselectronicclassroom.com)  
 Frequency Chart ; Bode Plot




- Open loop gain is about 2 at 2 Htz rolls of at a factor of ten as frequency is increased by a factor of 10 or 10 Db per octave ( Meaning gain drops by  $\frac{1}{2}$  when frequency dbls)
- Close loop gain is 100 roll off starts at 10 khz, then continues to Roll off at the same rate as open loop gain.

Slew Rate


FAIRCHILD LINEAR INTEGRATED CIRCUITS $\mu A741C$					
ELECTRICAL CHARACTERISTICS ( $V_s = \pm 15V$ , $T_A = 25^\circ C$ unless otherwise specified)					
PARAMETERS (see definitions)	CONDITIONS	MIN.	TYP.	MAX.	UNITS
Input Offset Voltage	$R_L \leq 10k\Omega$		2.0	6.0	mV
Input Offset Current			20	200	nA
Input Bias Current			80	500	nA
Input Resistance		0.3	2.0		M $\Omega$
Input Capacitance			1.4		pF
Offset Voltage Adjustment Range			$\pm 15$		mV
Input Voltage Range		$\pm 12$	$\pm 13$		V
Common Mode Rejection Ratio	$R_L \leq 10k\Omega$	70	90		dB
Supply Voltage Rejection Ratio	$R_L \leq 10k\Omega$		30	150	$\mu V/V$
Large-Signal Voltage Gain	$R_L \geq 2k\Omega$ , $V_{out} = \pm 10V$	20,000	200,000		
Output Voltage Swing	$R_L \geq 10k\Omega$	$\pm 12$	$\pm 13$		V
Output Resistance	$R_L \geq 2k\Omega$	$\pm 10$	75		$\Omega$
Output Short-Circuit Current			25		mA
Supply Current			1.7	2.8	mA
Power Consumption			50	85	mW
Transient Response (unity gain)	$V_{in} = 20mV$ , $R_L = 2k\Omega$ , $C_L \leq 100pF$				
Risetime			0.3		$\mu s$
Overshoot			5.0		%
Slew Rate	$R_L \geq 2k\Omega$		0.5		V/ $\mu s$
The following specifications apply for $0^\circ C \leq T_A \leq +70^\circ C$ :					
Input Offset Voltage				7.5	mV
Input Offset Current				300	nA
Input Bias Current				800	nA
Large-Signal Voltage Gain	$R_L \geq 2k\Omega$ , $V_{out} = \pm 10V$	15,000			
Output Voltage Swing	$R_L \geq 2k\Omega$	$\pm 10$	$\pm 13$		V

### Slew Rate

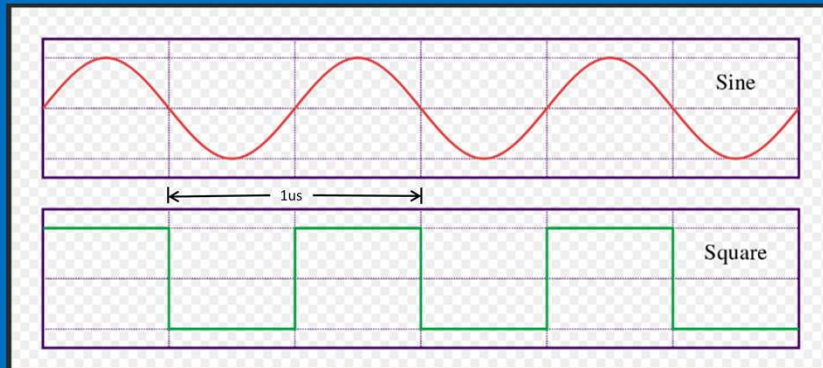

- Slew rate is the Rise Time of the operational amplifier. This specification is important when there is a large voltage swing on a Square wave.
- The slew Rate for the above Wave Forms is  $0.5\text{v} / \mu\text{s}$ .
- If my frequency above is 1 Mhz and the Wave form has a peak Voltage of 1 v peak


### Slew Rate

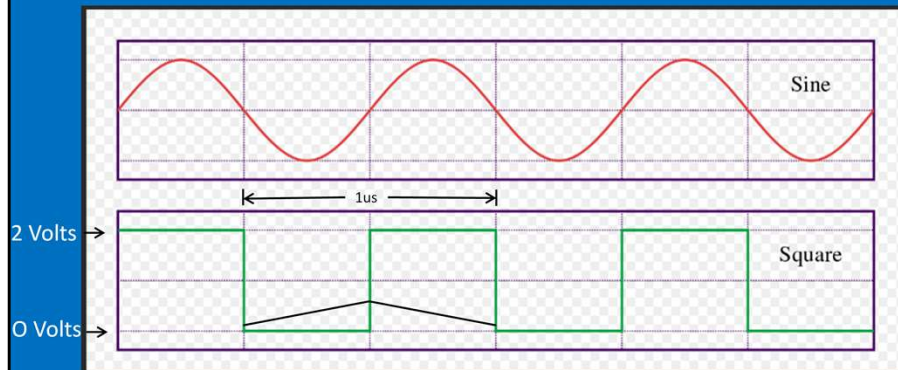


- Slew rate is the Rise Time of the operational amplifier. This specification is important when there is a large voltage swing on a Square wave.
- The slew Rate for the above Wave Forms is  $0.5\text{v} / \mu\text{s}$ .
- If my frequency above is 1 Mhz and the Wave form has a peak Voltage of 2 v peak



### Linear Op Amp Summary

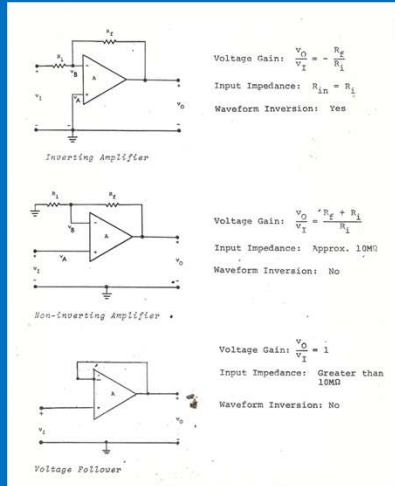

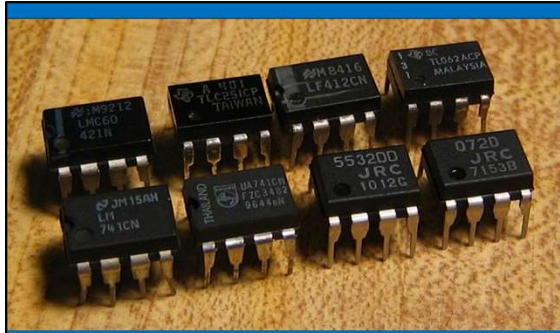- Voltage Gain =  $V_i = -\frac{R_f}{R_i}$
  - Input Impedance =  $R_i$
  - Inversion yes = input; output by 180 degrees
- 
- Voltage Gain =  $V_i = 1 + \frac{R_f}{R_i}$
  - Input Impedance = High Input Impedance
  - Inversion no = input; output in Phase
- 
- Voltage Gain = 1
  - Input Impedance = High Input Impedance
  - Inversion no = input; output in Phase



## Continue to Part two Differential Operational Amplifier

Operational Amplifiers from Soup to Nuts  
AI's Electronic Class Room

## The Greatest Operational Amplifier Course on the Internet.



Al's Electronic Class Room  
[www.alselectronicclassroom.com](http://www.alselectronicclassroom.com)