
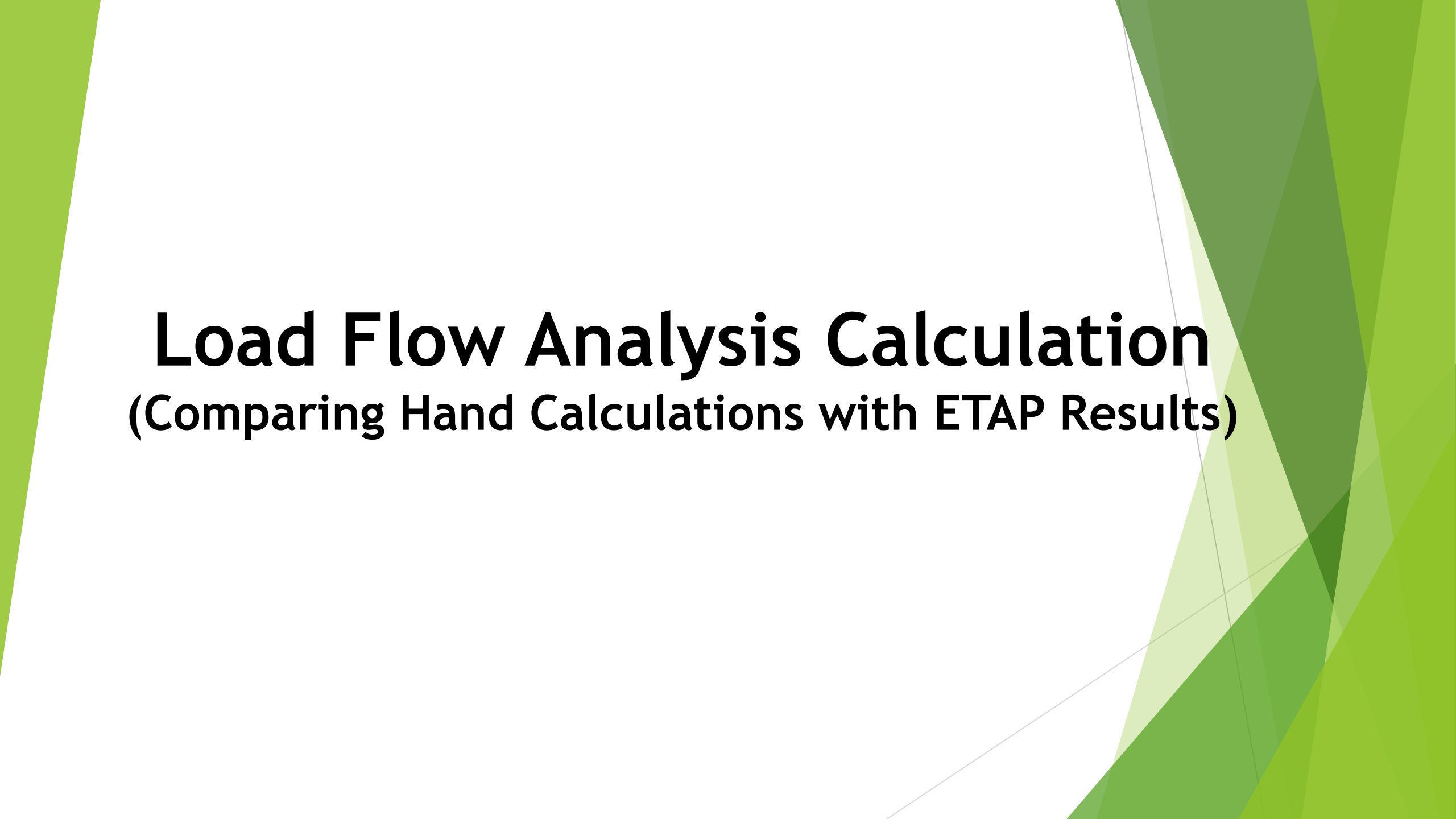


The background features abstract, overlapping green geometric shapes, primarily triangles and polygons, in various shades of green, creating a modern and dynamic look.


Load Flow Analysis Calculation

(Comparing Hand Calculations with ETAP Results)

How Load Flow Calculation Works?

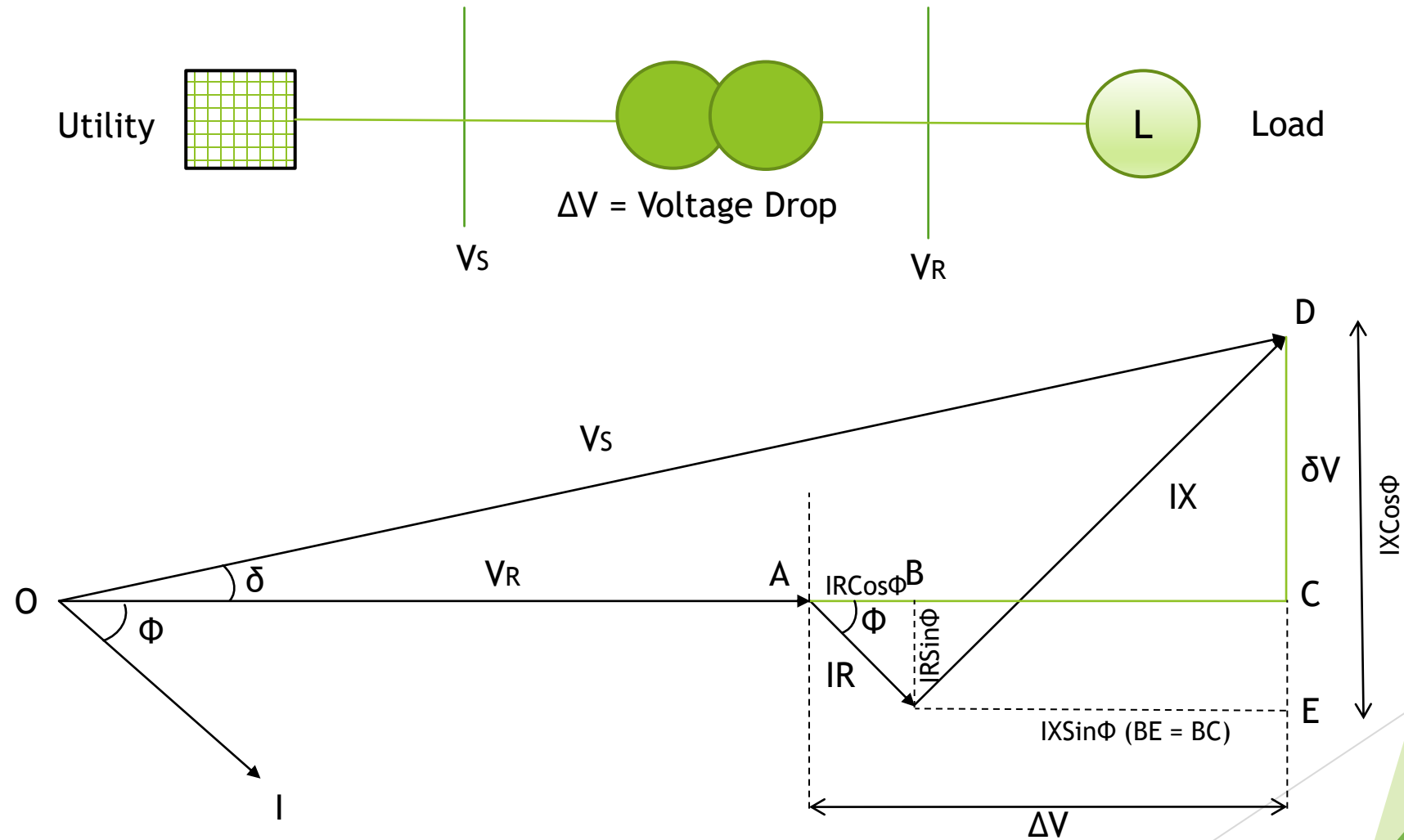

How Load Flow Calculation Works?

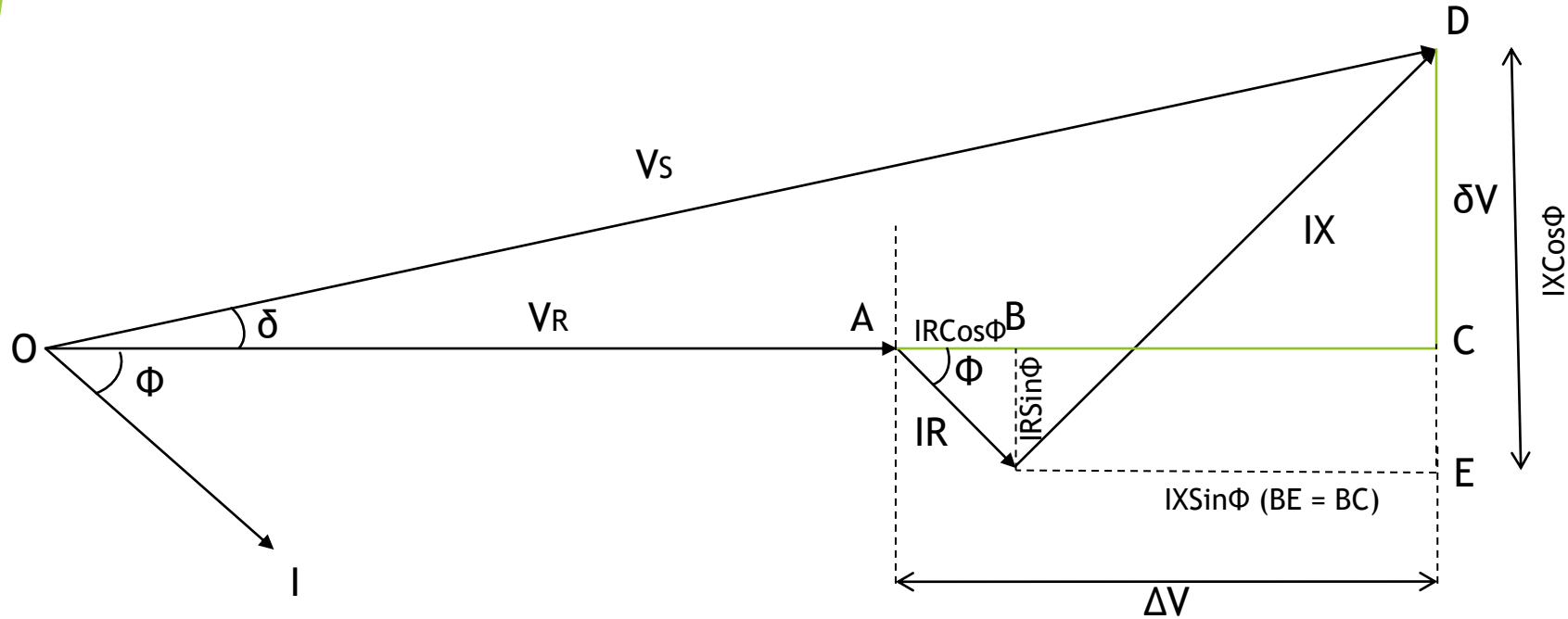

$$OD = V_S, OA = V_R$$

$$OD^2 = OC^2 + CD^2$$


$$OD^2 = (OA + AB + BC)^2 + (DE - CE)^2$$

$$AB = IR \cos \phi, BC = IX \sin \phi$$

$$DE = IX \cos \phi, CE = IR \sin \phi$$

$$\begin{aligned} V_S^2 &= (V_R + IR \cos \phi + IX \sin \phi)^2 + (IX \cos \phi - IR \sin \phi)^2 \\ &= (V_R + (R^*P + X^*Q)/V_R)^2 + (X^*P - R^*Q)/V_R^2 \\ V_S &= \sqrt{\{(V_R + (R^*P + X^*Q)/V_R)^2 + (X^*P - R^*Q)/V_R^2\}} \\ \tan \delta &= CD / OC = (DE - CE) / (OA + AB + BC) \\ &= (IX \cos \phi - IR \sin \phi) / (V_R + IR \cos \phi + IX \sin \phi) \\ &= ((X^*P - R^*Q)/V_R) / (V_R + (R^*P + X^*Q)/V_R) \\ \delta &= \text{ATAN} [((X^*P - R^*Q)/V_R) / (V_R + (R^*P + X^*Q)/V_R)] \text{ Radian} \end{aligned}$$

How Load Flow Calculation Works?

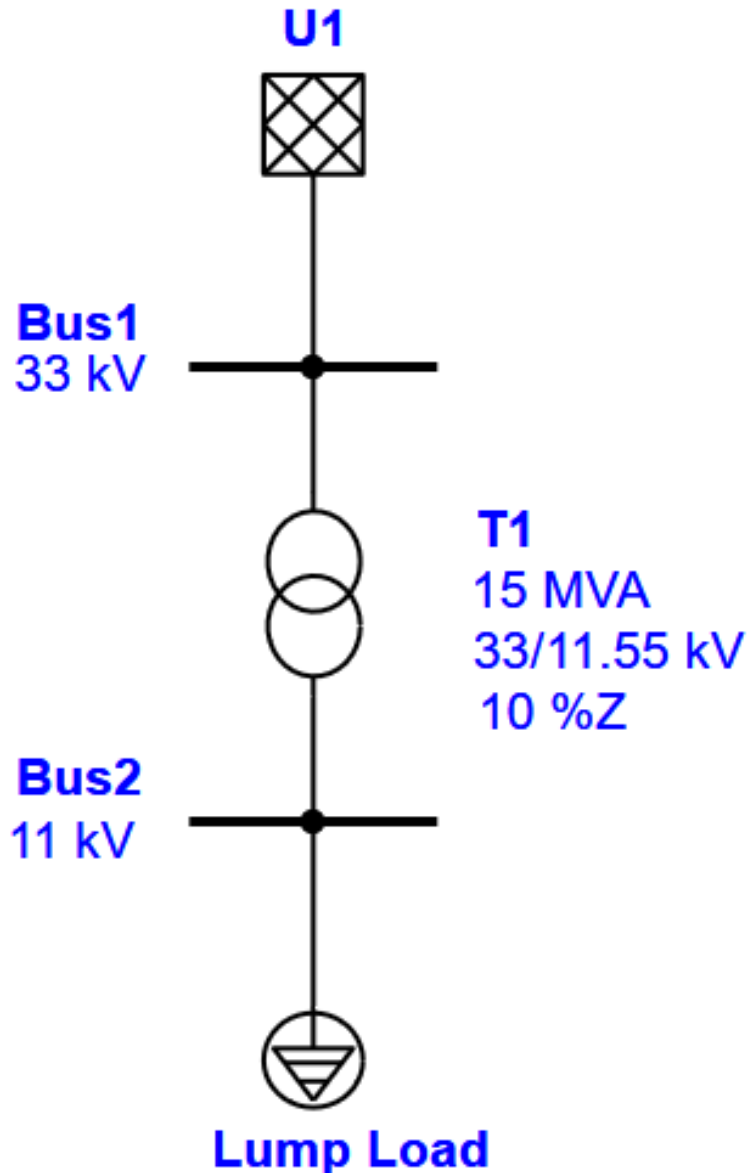

Grid Data

Grid Voltage = 33kV

Bus Data

Bus Voltage = 33kV

Transformer Data

Voltage Rating - 33/11.55 kV

MVA Rating - 15 MVA

% Impedance - 10%

X/R Ratio - 18.6

Load Data

Voltage Rating - 11 kV, MVA Rating - 12 MVA

Motor Load - 80%, Static Load - 20%

Power Factor - 80%